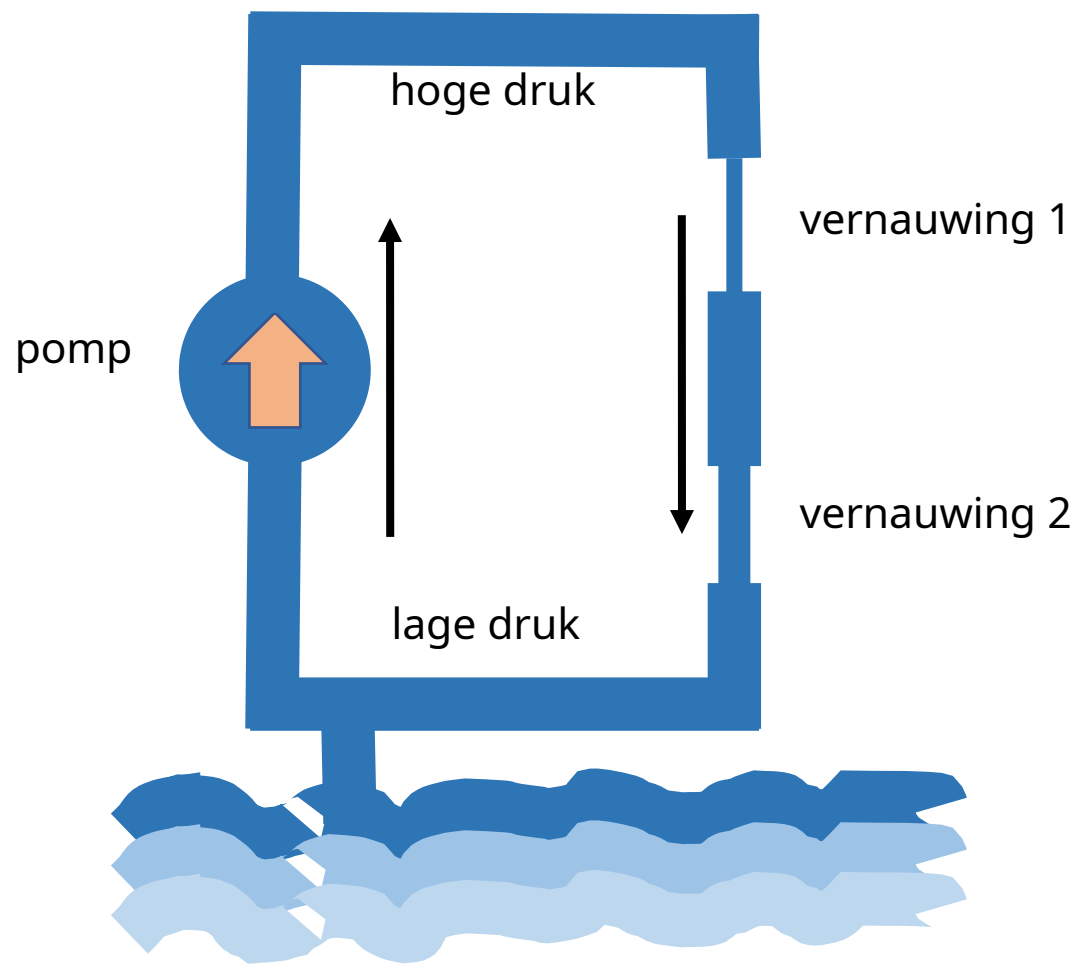







Uitgelegd met behulp van water


Spanning, stroom en weerstand






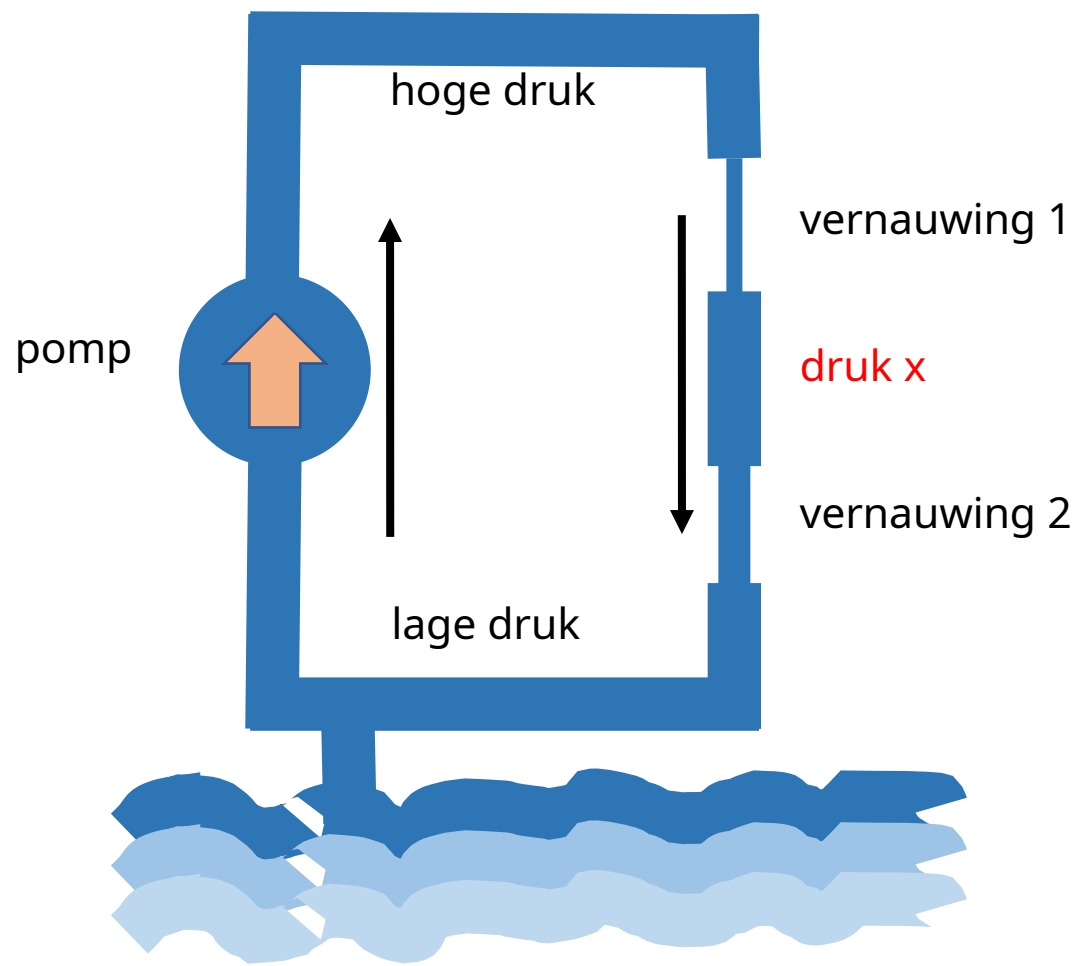


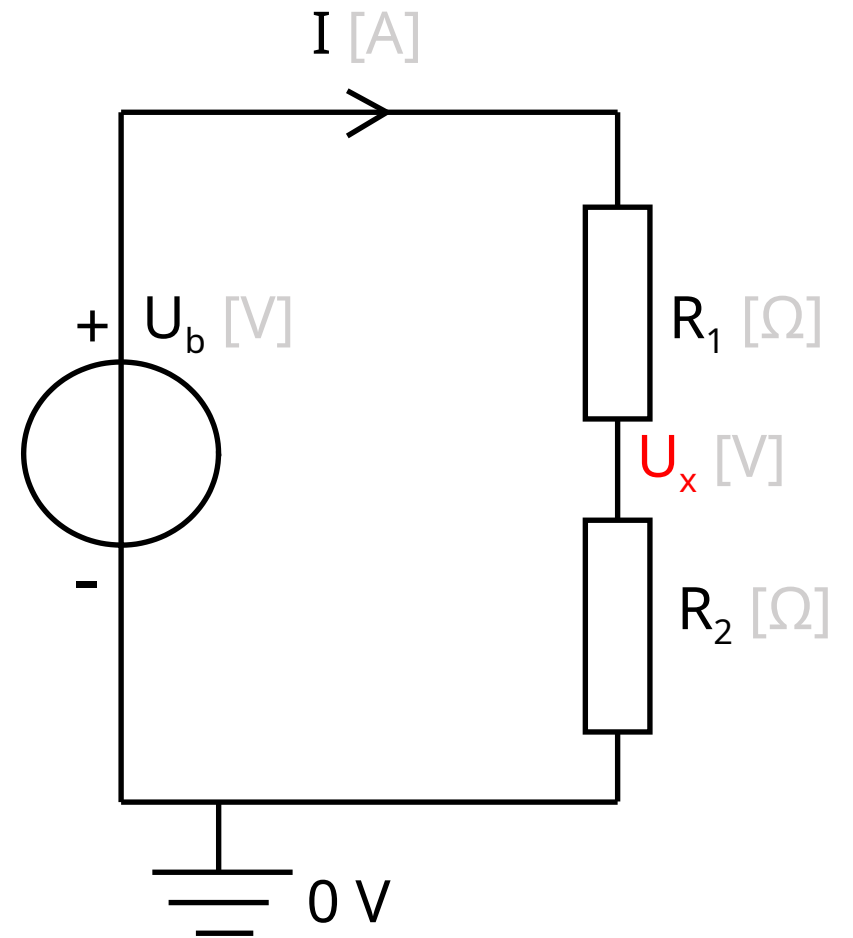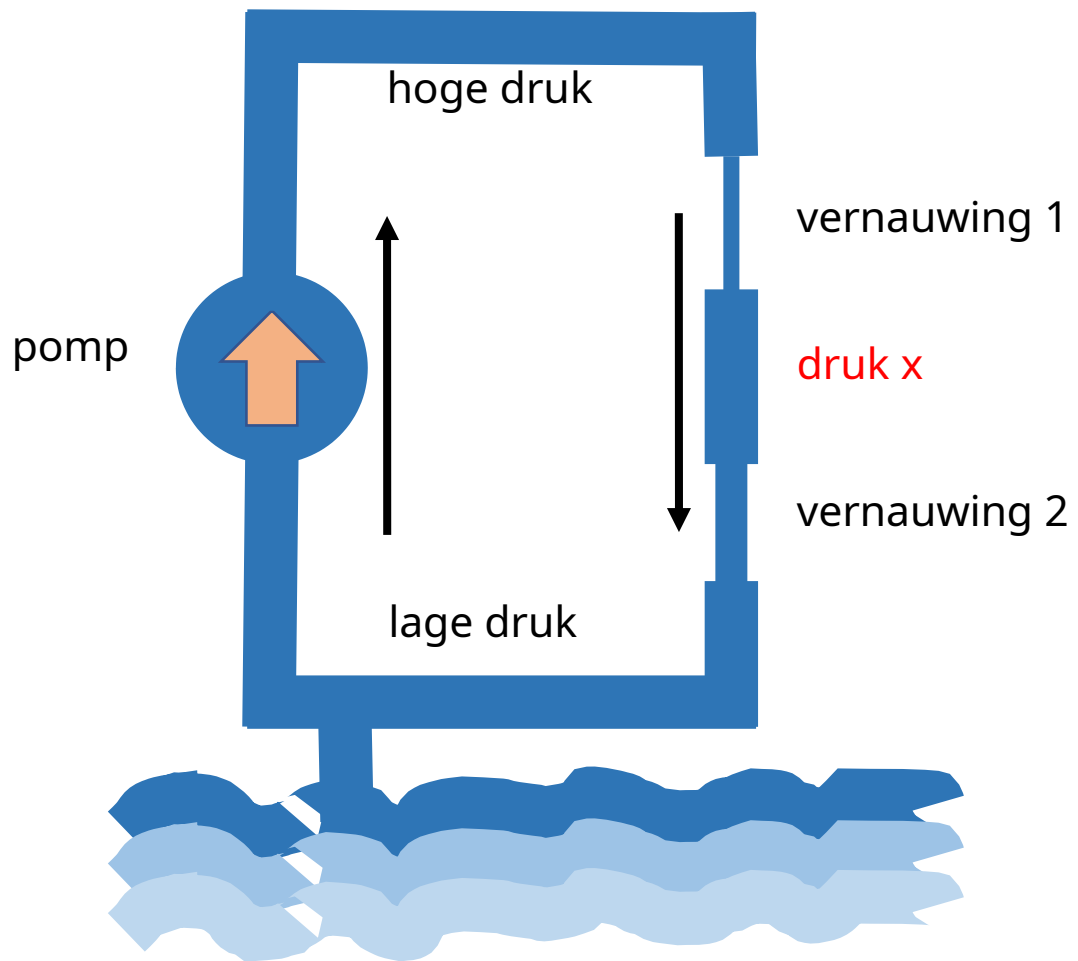

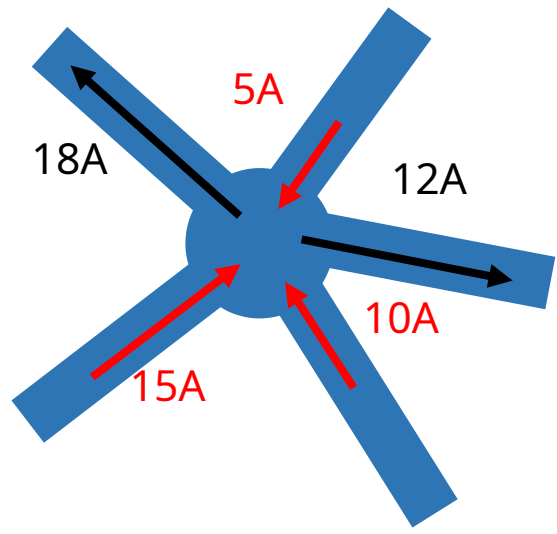


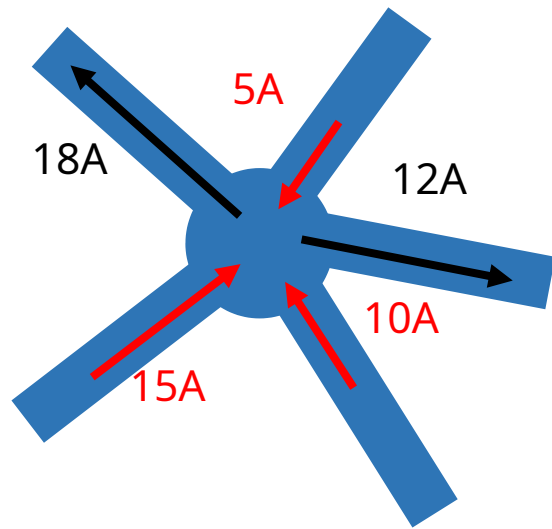


$$5 + 10 + 15 = 18 + 12$$

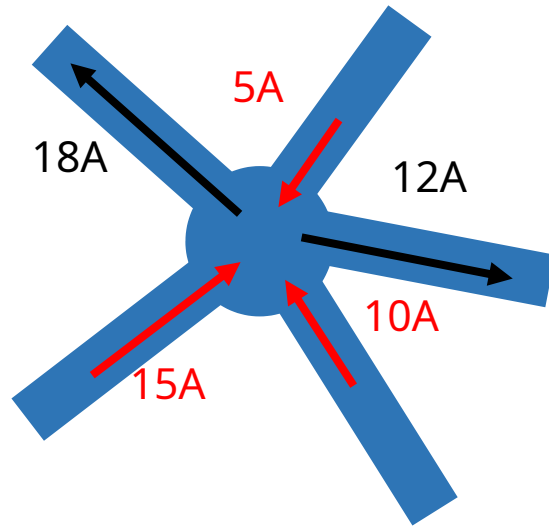

$$5 + 10 + 15 = 18 + 12 \quad | \quad + -18 + -12$$

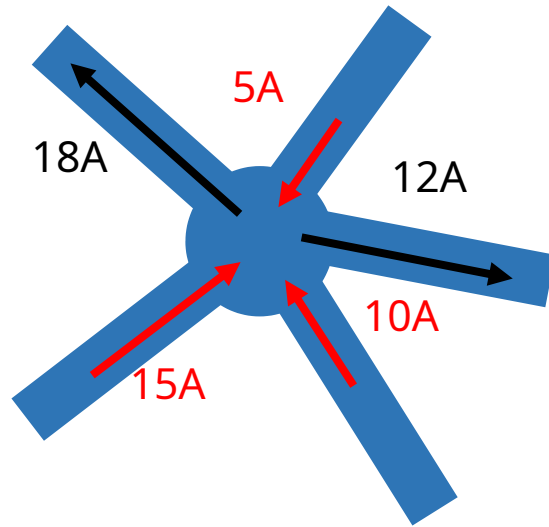

$$5 + 10 + 15 = 18 + 12 \quad | \quad + -18 + -12$$
$$5 + 10 + 15 + -18 + -12 = 0$$

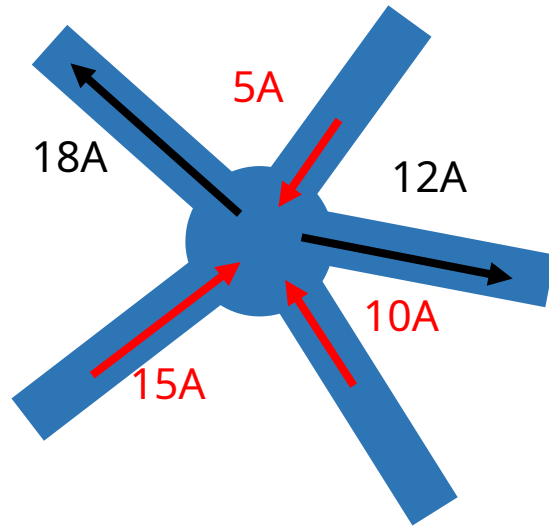



$$5 + 10 + 15 = 18 + 12 \quad | \quad + -18 + -12$$
$$5 + 10 + 15 + -18 + -12 = 0$$

1e wet van
Kirchhoff:


$$\sum I = 0$$

op elk knooppunt

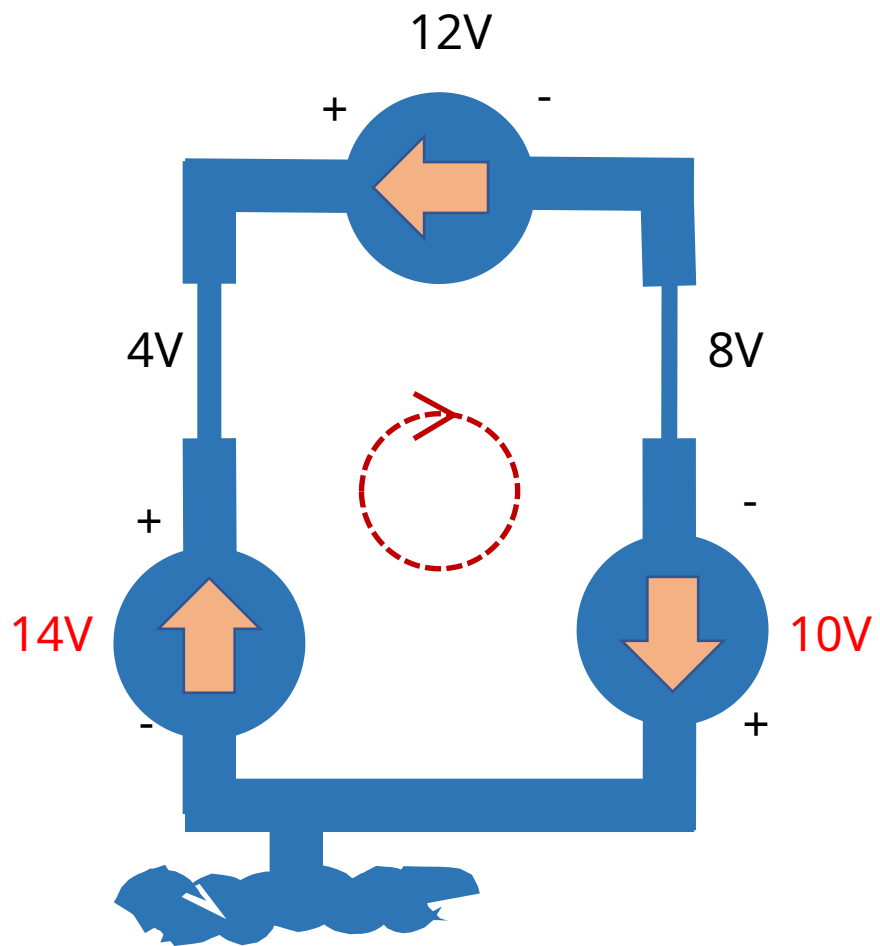

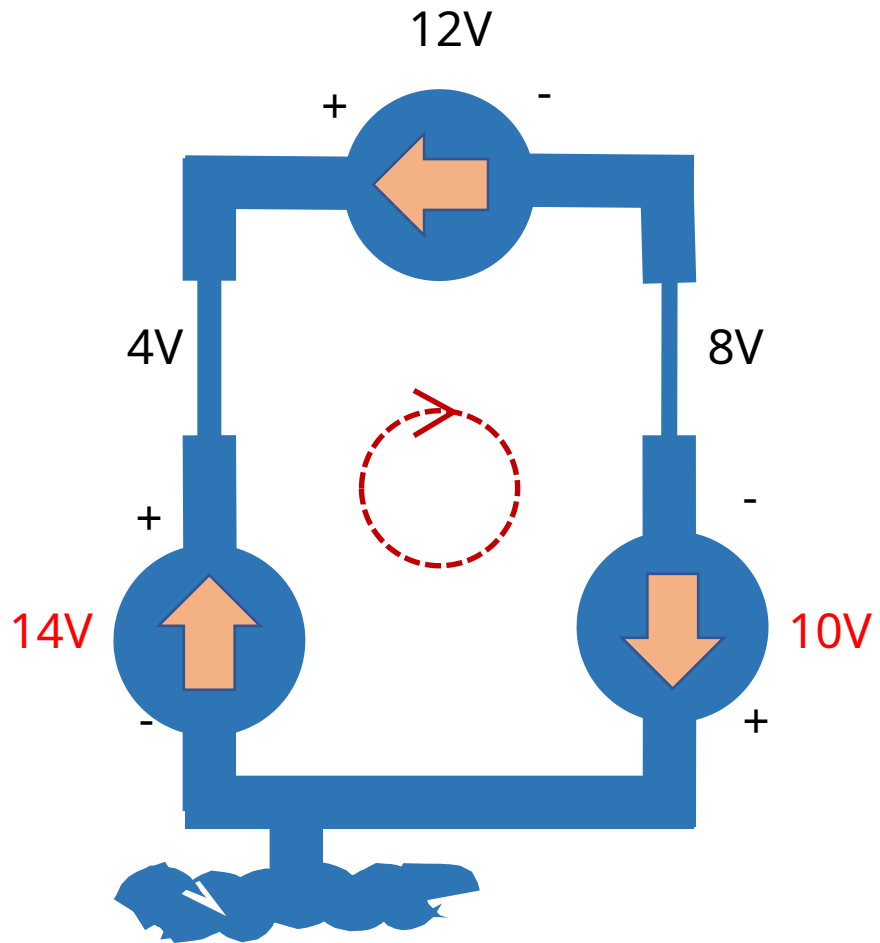

$$14 + 10 + -4 + -12 + -8 = 0$$

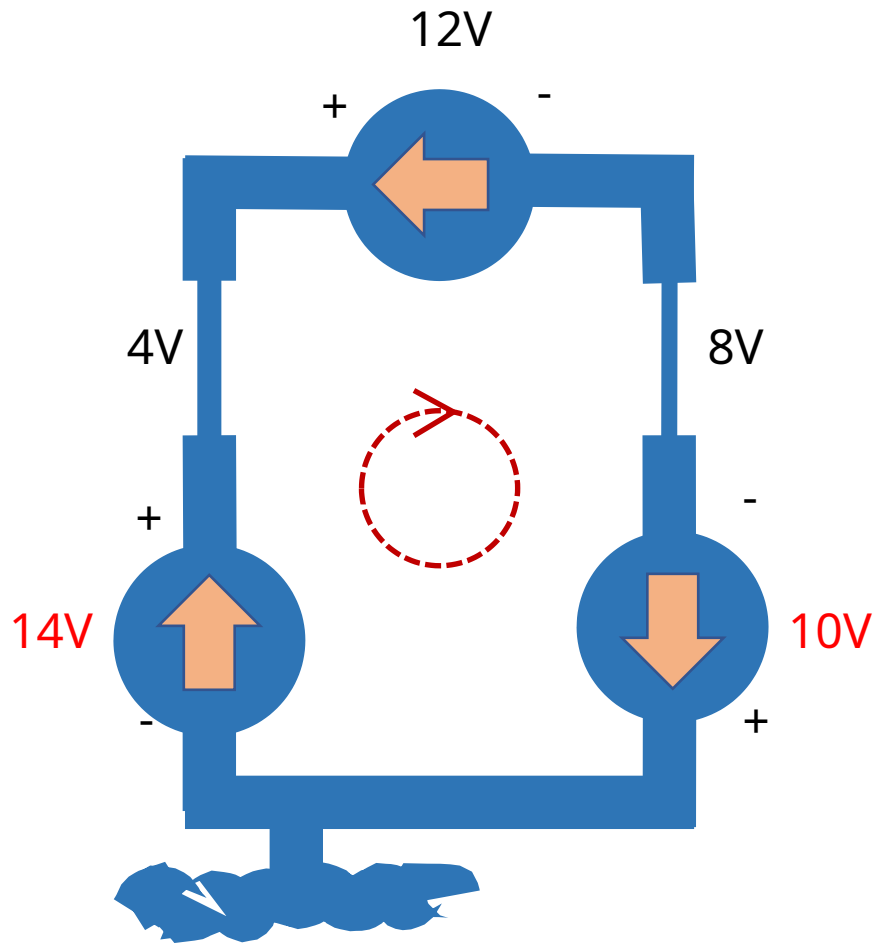


$$14 + 10 + -4 + -12 + -8 = 0$$

2e wet van
Kirchhoff:

$$\sum U = 0$$

in elke lus

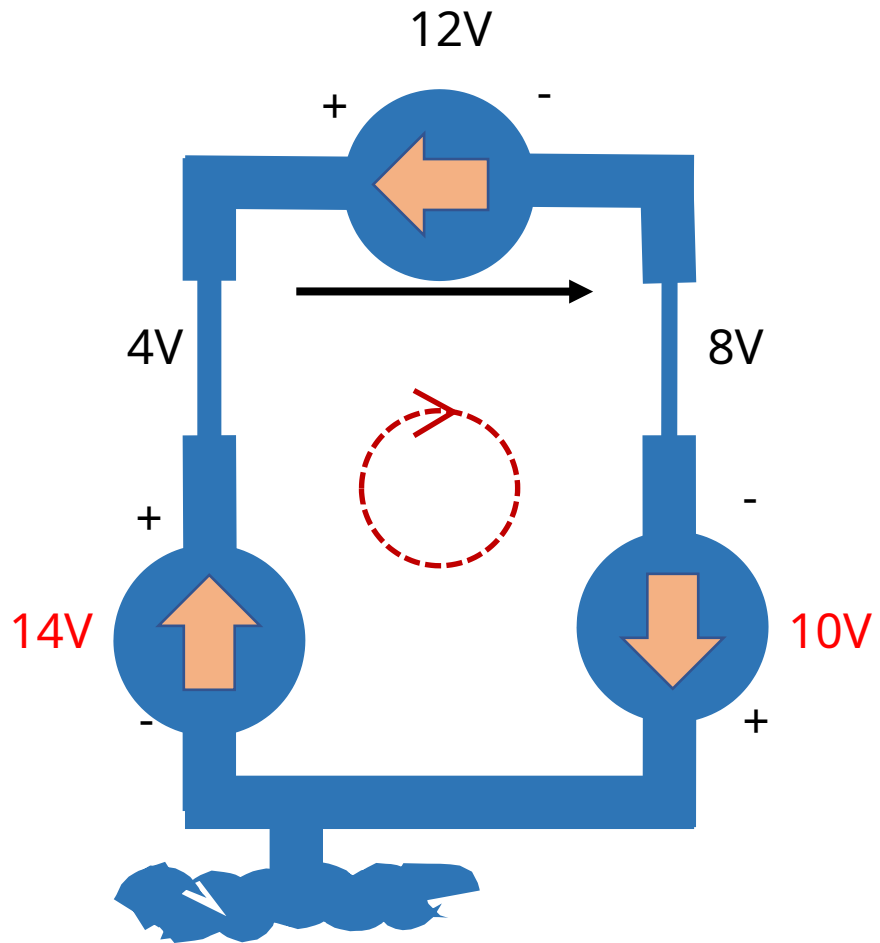


$$14 + 10 + -4 + -12 + -8 = 0$$

2e wet van Kirchhoff:

$$\sum U = 0$$

in elke lus

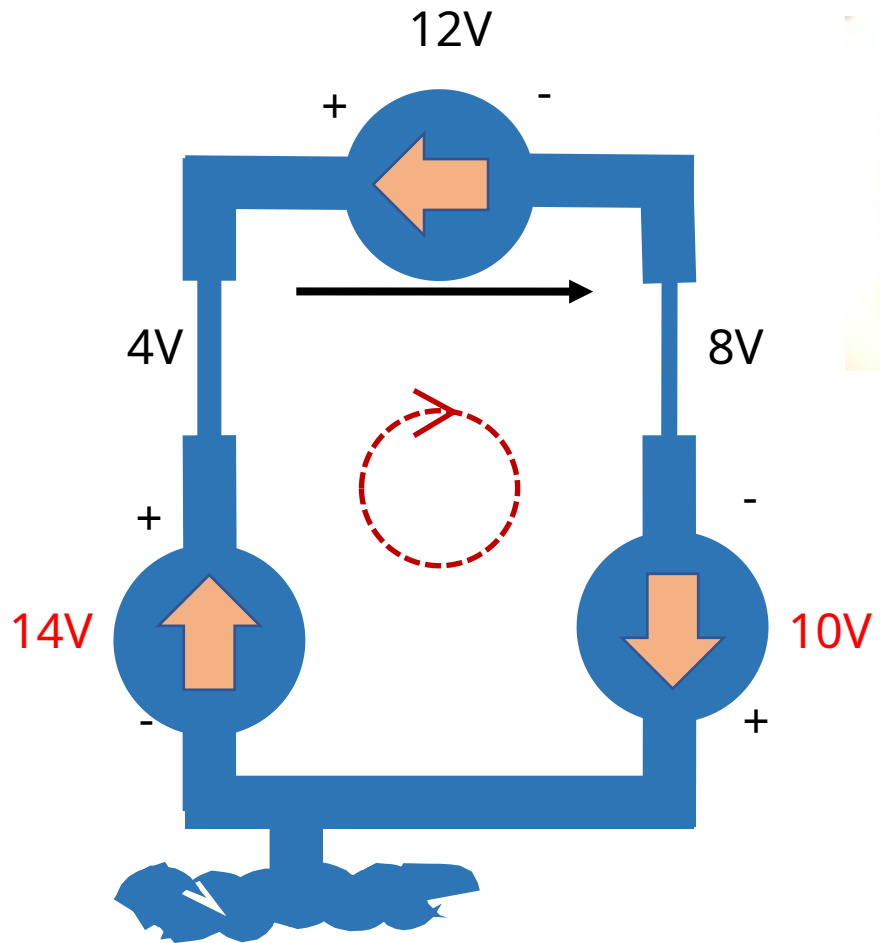




2e wet van
Kirchhoff:



$$\sum U = 0$$



in elke lus

$$14 + 10 + -4 + -12 + -8 = 0$$

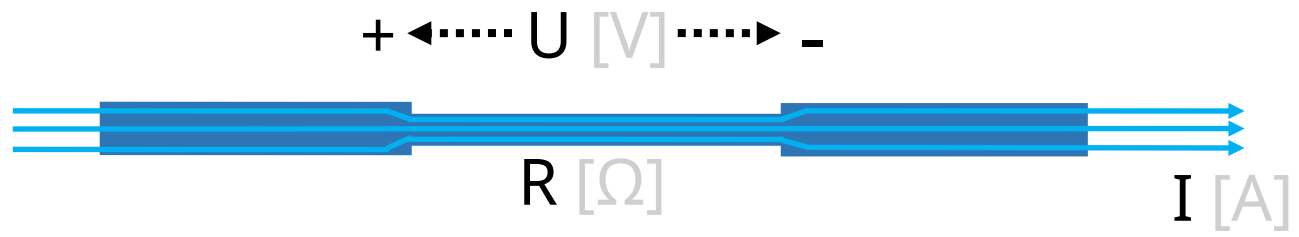

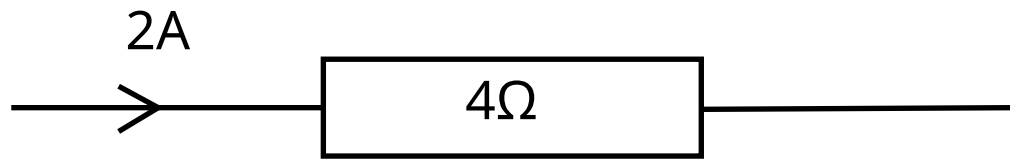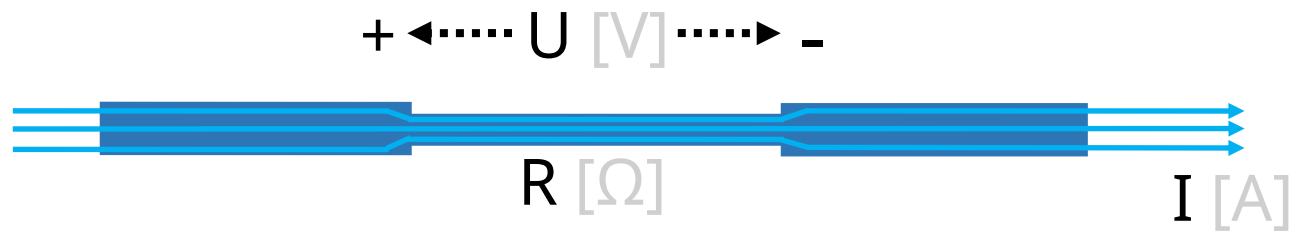

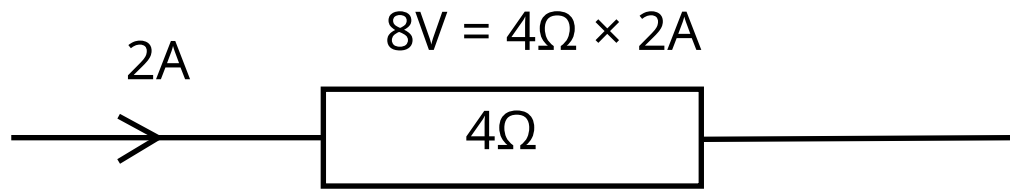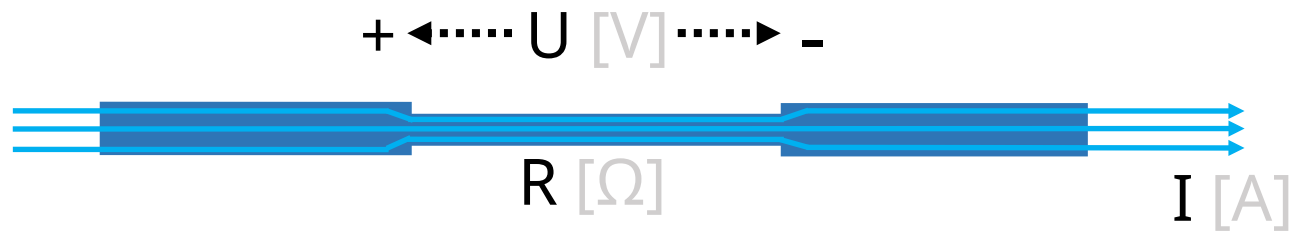


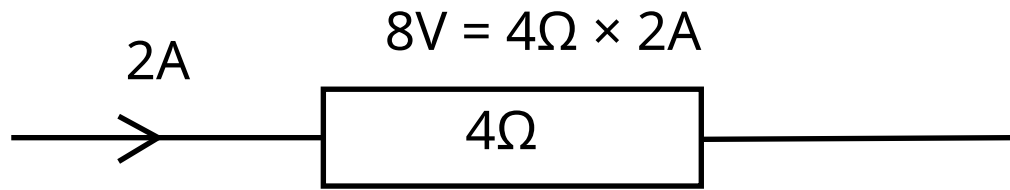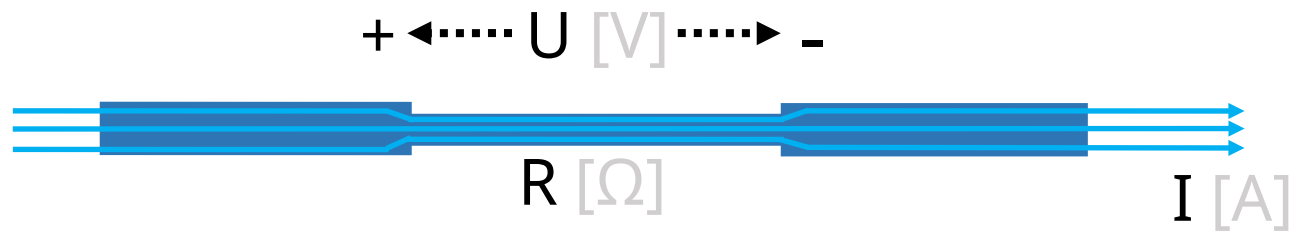


Wet van Ohm:

$$U = RI$$


voor elke
weerstand

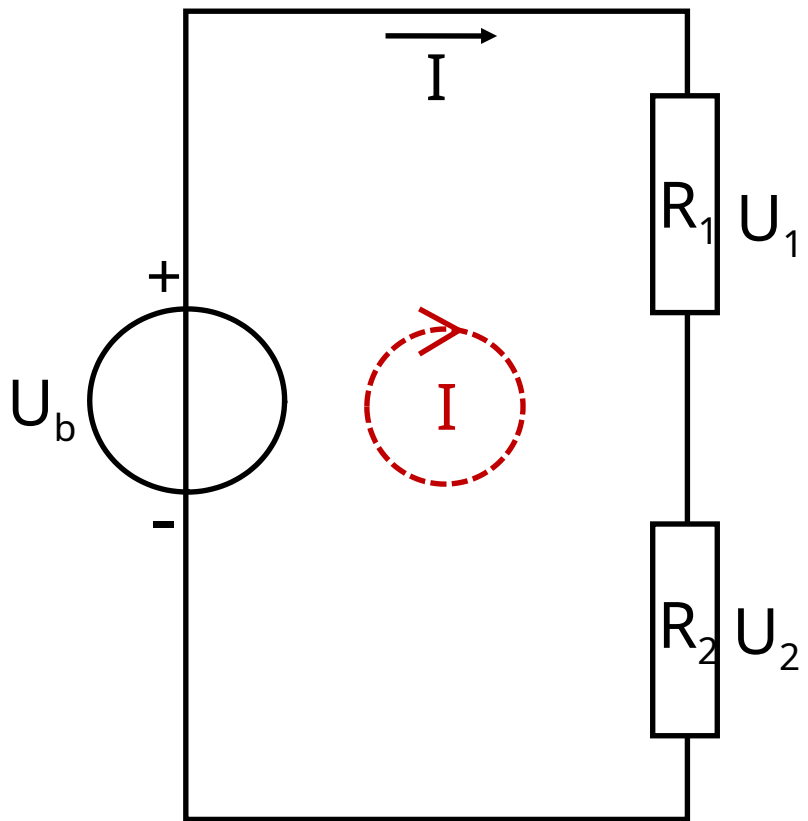

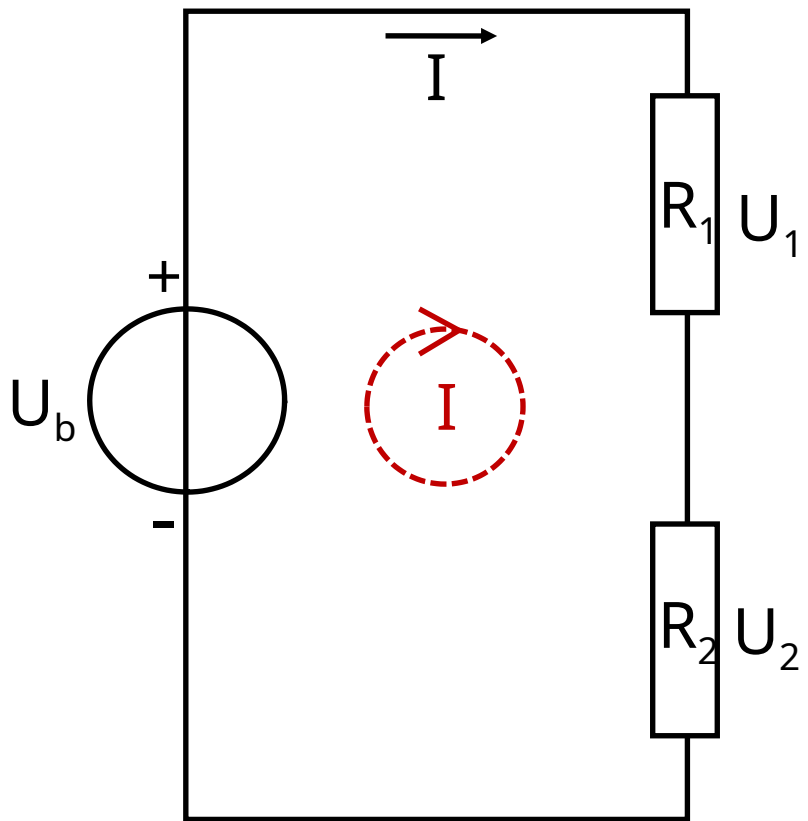

K2:
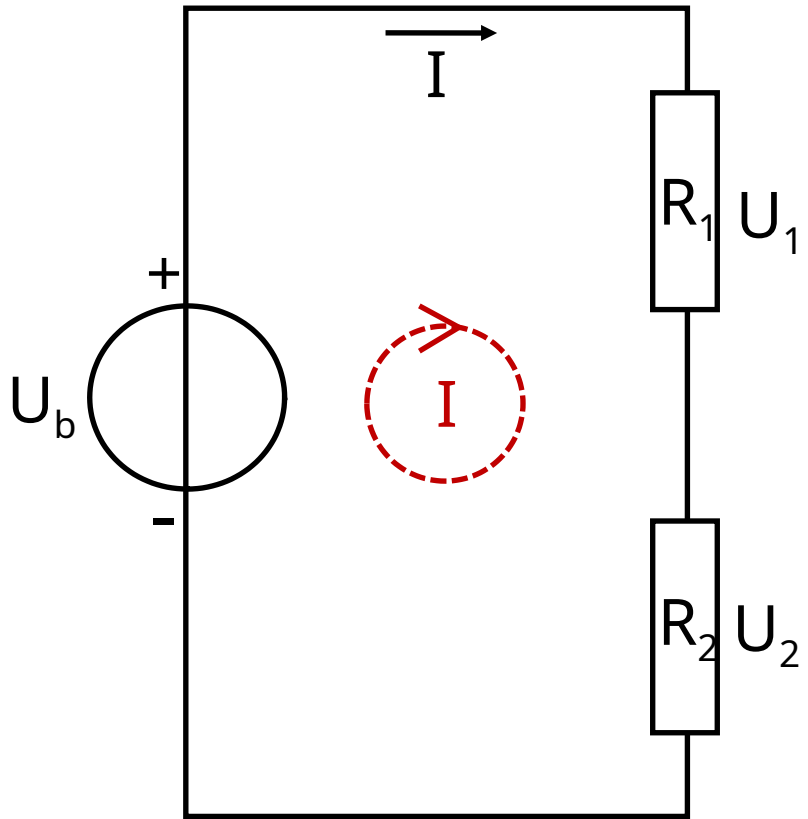
$$U_b + -U_1 + -U_2 = 0 \Rightarrow U_b = U_1 + U_2$$




K2:

$$U_b + -U_1 + -U_2 = 0 \Rightarrow U_b = U_1 + U_2$$

Ohm:

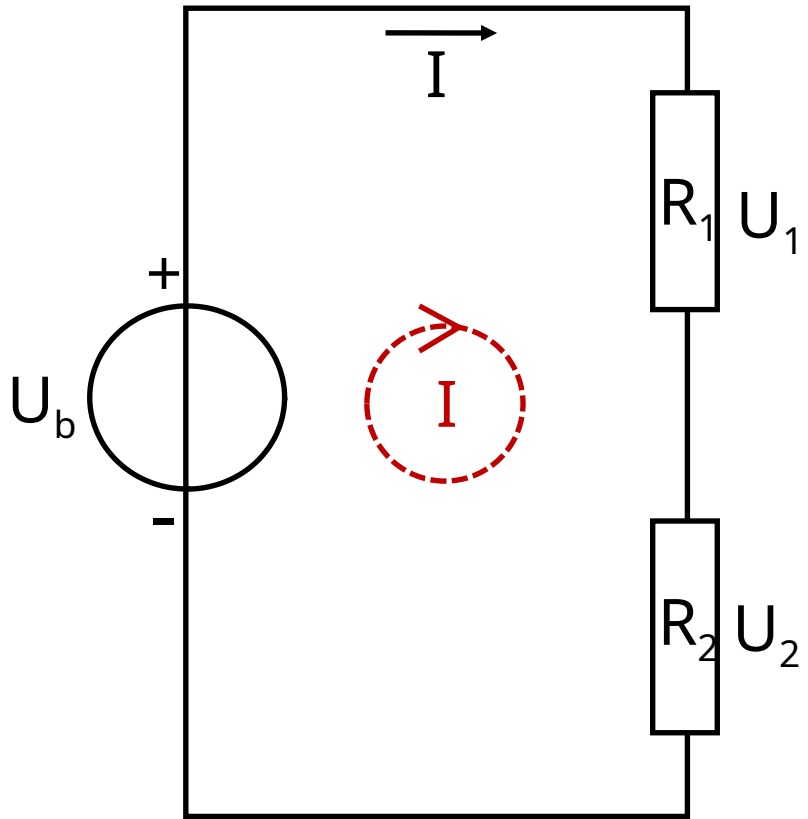
$$U_1 = R_1 I \quad \wedge \quad U_2 = R_2 I$$



K2: $U_b + -U_1 + -U_2 = 0 \Rightarrow U_b = U_1 + U_2$

Ohm: $U_1 = R_1 I \quad \wedge \quad U_2 = R_2 I$

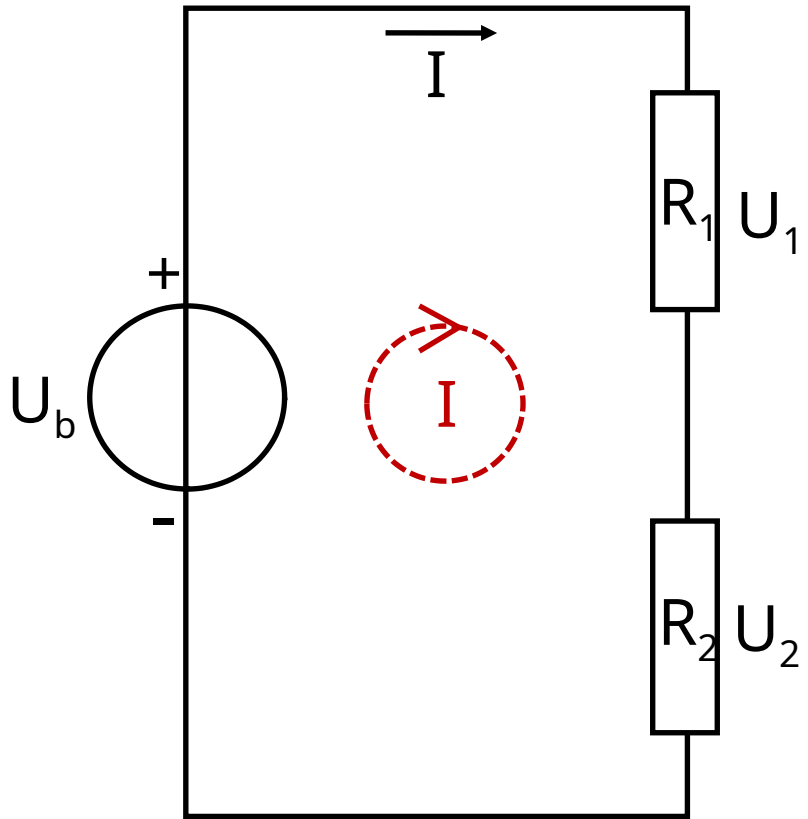K2 \wedge Ohm $\Rightarrow U_b = R_1 I + R_2 I$




K2: $U_b + -U_1 + -U_2 = 0 \Rightarrow U_b = U_1 + U_2$

Ohm: $U_1 = R_1 I \quad \wedge \quad U_2 = R_2 I$

K2 \wedge Ohm $\Rightarrow U_b = R_1 I + R_2 I$

$\Rightarrow U_b = (R_1 + R_2) I$

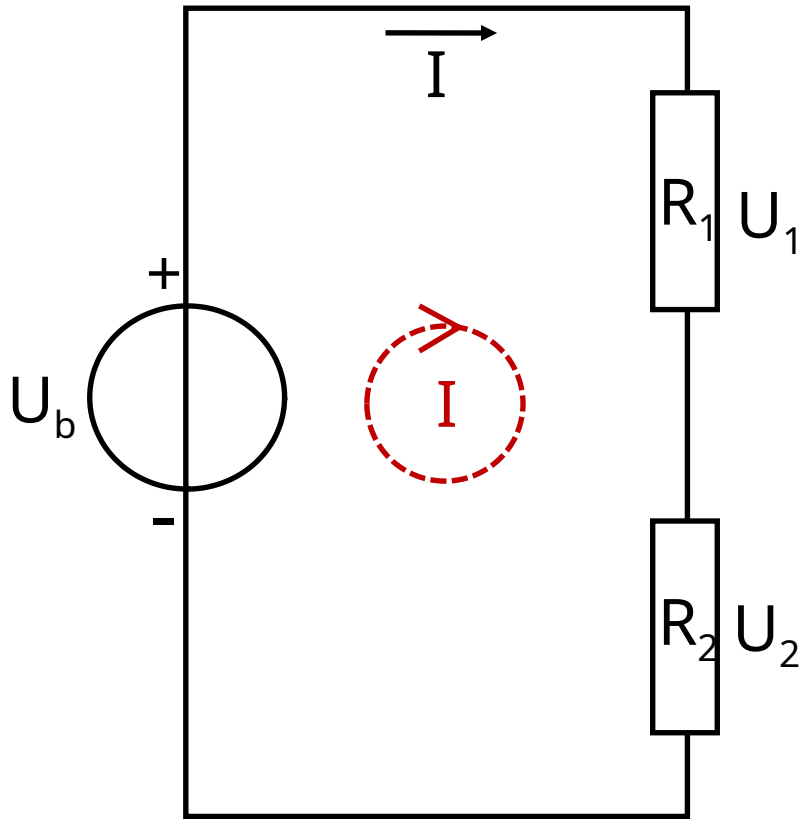


K2: $U_b + -U_1 + -U_2 = 0 \Rightarrow U_b = U_1 + U_2$

Ohm: $U_1 = R_1 I \quad \wedge \quad U_2 = R_2 I$

K2 \wedge Ohm $\Rightarrow U_b = R_1 I + R_2 I$

$\Rightarrow U_b = (R_1 + R_2) I \quad \Bigg| \quad \times \frac{1}{R_1 + R_2}$

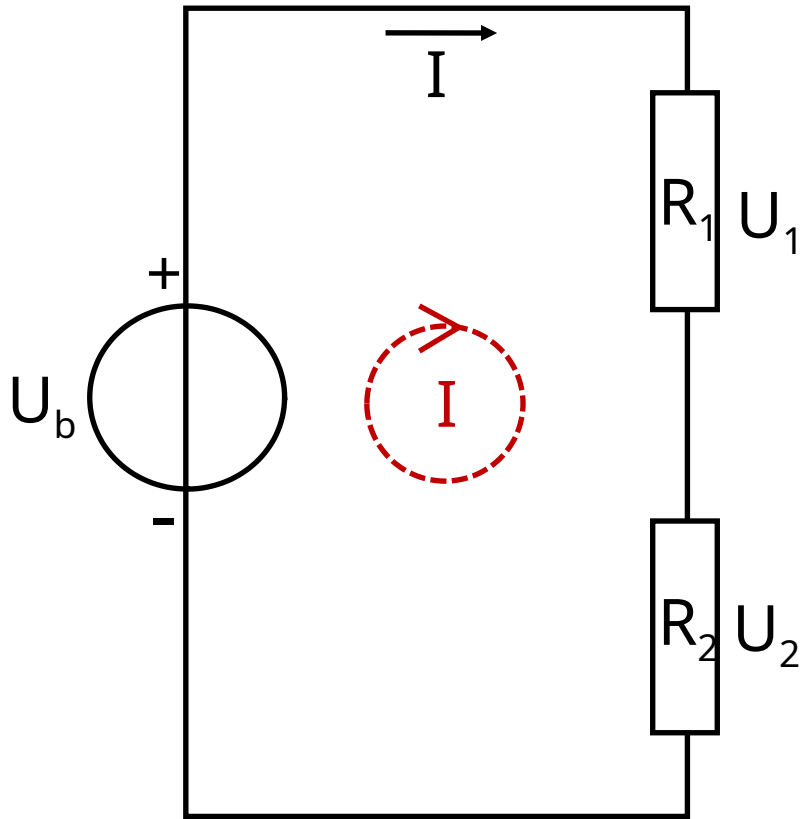


K2: $U_b + -U_1 + -U_2 = 0 \Rightarrow U_b = U_1 + U_2$

Ohm: $U_1 = R_1 I \quad \wedge \quad U_2 = R_2 I$

K2 \wedge Ohm $\Rightarrow U_b = R_1 I + R_2 I$

$\Rightarrow U_b = (R_1 + R_2) I \quad \left| \times \frac{1}{R_1 + R_2} \right.$

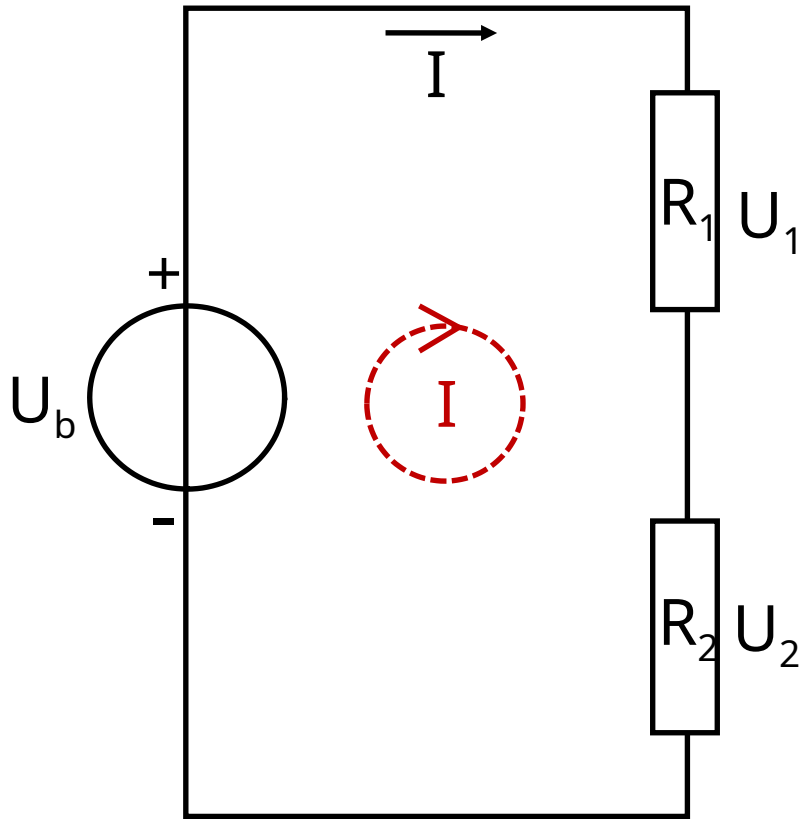$\Rightarrow I = \frac{1}{R_1 + R_2} U_b$




K2: $U_b + -U_1 + -U_2 = 0 \Rightarrow U_b = U_1 + U_2$

Ohm: $U_1 = R_1 I \quad \wedge \quad U_2 = R_2 I$

K2 \wedge Ohm $\Rightarrow U_b = R_1 I + R_2 I$

$\Rightarrow U_b = (R_1 + R_2) I \quad \left| \times \frac{1}{R_1 + R_2} \right.$

$\Rightarrow I = \frac{1}{R_1 + R_2} U_b \quad \left| \text{Ohm} \right.$

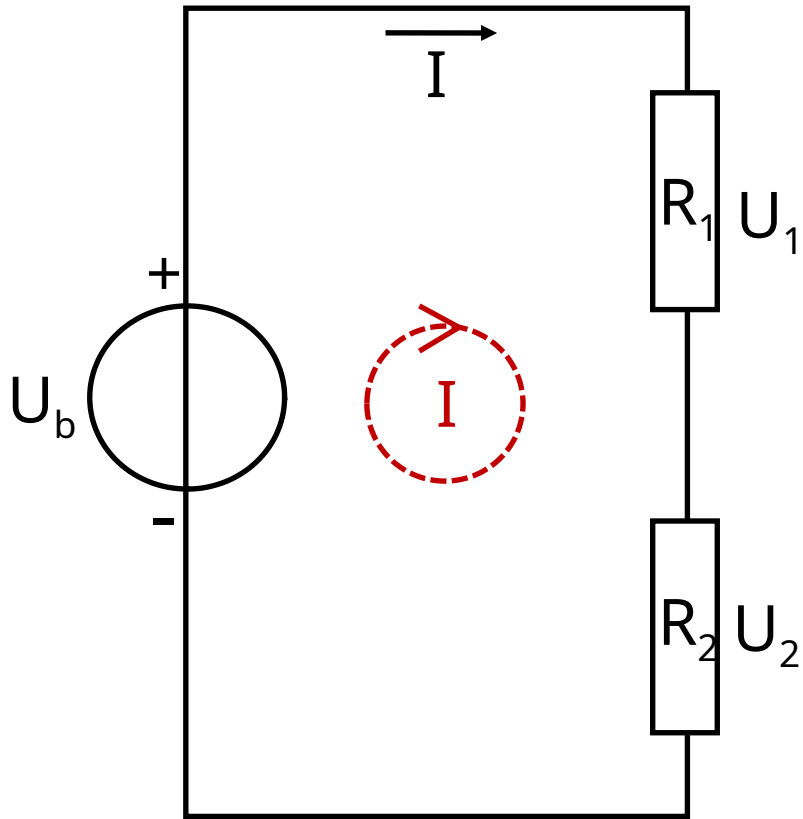

K2: $U_b + -U_1 + -U_2 = 0 \Rightarrow U_b = U_1 + U_2$


Ohm: $U_1 = R_1 I \quad \wedge \quad U_2 = R_2 I$

K2 \wedge Ohm $\Rightarrow U_b = R_1 I + R_2 I$

$\Rightarrow U_b = (R_1 + R_2) I$ $\left| \times \frac{1}{R_1 + R_2} \right.$

$\Rightarrow I = \frac{1}{R_1 + R_2} U_b$ $\left| \text{Ohm} \right.$

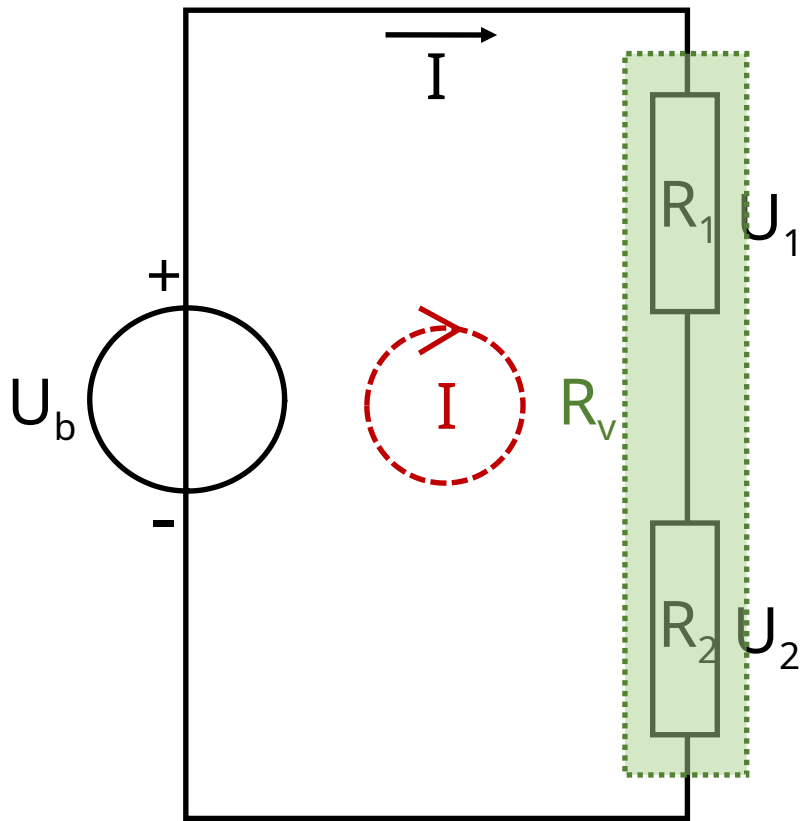$\Rightarrow U_1 = \frac{R_1}{R_1 + R_2} U_b \quad \wedge \quad U_2 = \frac{R_2}{R_1 + R_2} U_b$



K2: $U_b + -U_1 + -U_2 = 0 \Rightarrow U_b = U_1 + U_2$

Ohm: $U_1 = R_1 I \quad \wedge \quad U_2 = R_2 I$


K2 \wedge Ohm $\Rightarrow U_b = R_1 I + R_2 I$

$\Rightarrow U_b = \underbrace{(R_1 + R_2)}_{R_v} I \quad \left| \times \frac{1}{R_1 + R_2} \right.$


$\Rightarrow I = \frac{1}{R_1 + R_2} U_b \quad \left| \text{Ohm} \right.$

$\Rightarrow U_1 = \frac{R_1}{R_1 + R_2} U_b \quad \wedge \quad U_2 = \frac{R_2}{R_1 + R_2} U_b$

Spanningsdeler

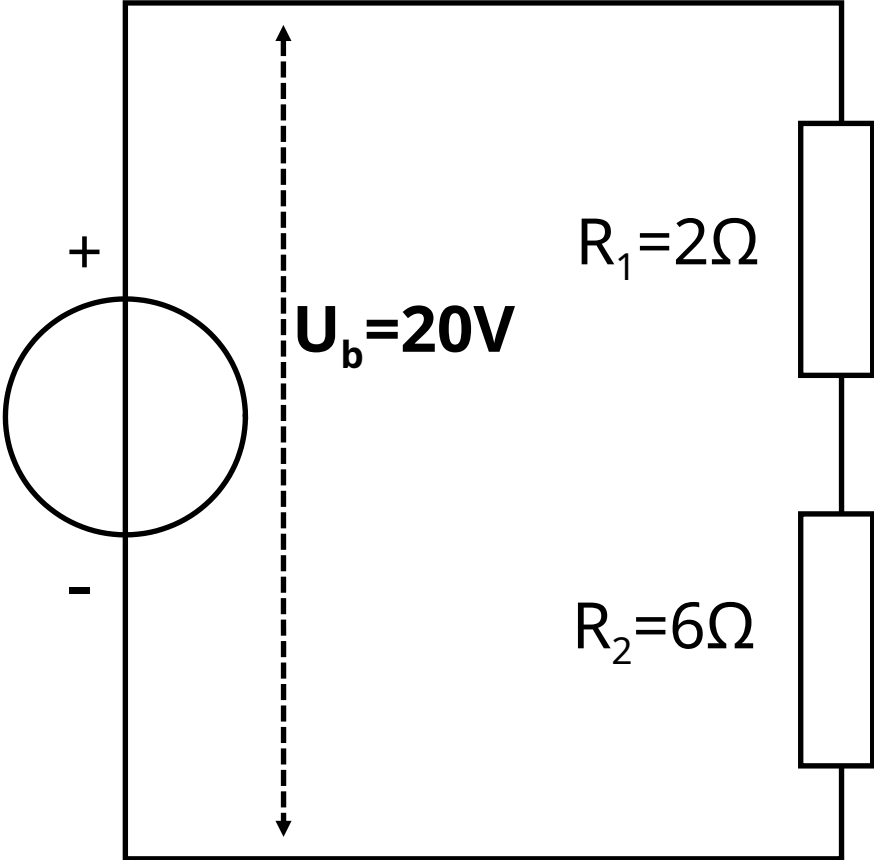


Spanningsdeler

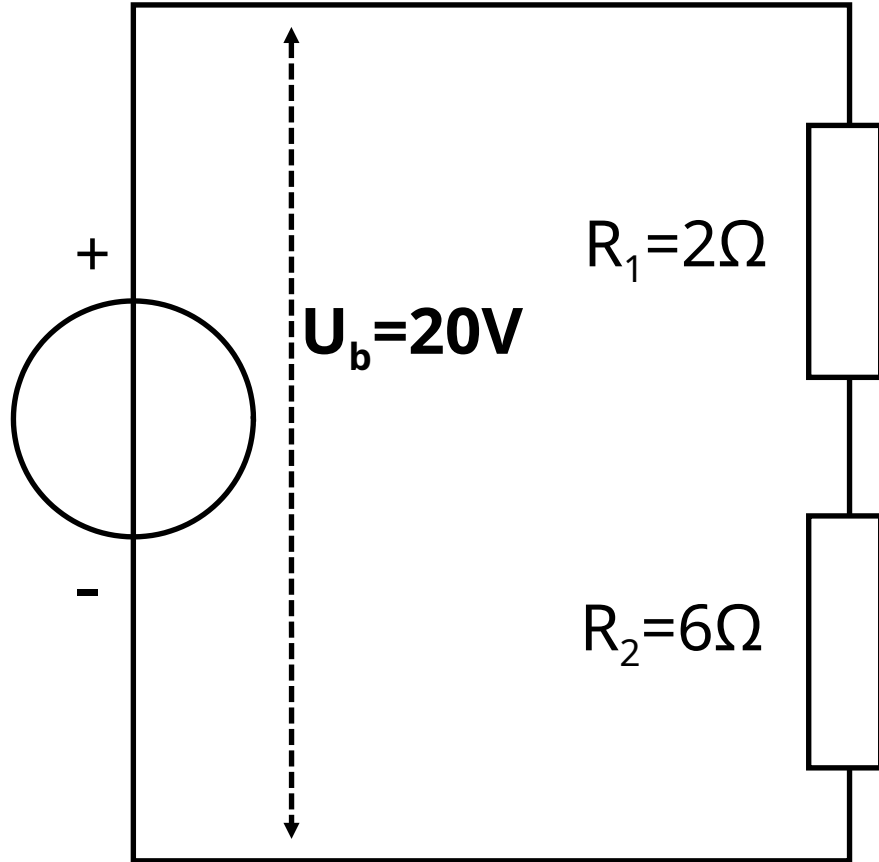

$$U_2 = \frac{R_2}{R_1 + R_2} U_b = \frac{6}{2 + 6} \times 20 \text{ V} = \mathbf{15V}$$


Spanningsdeler

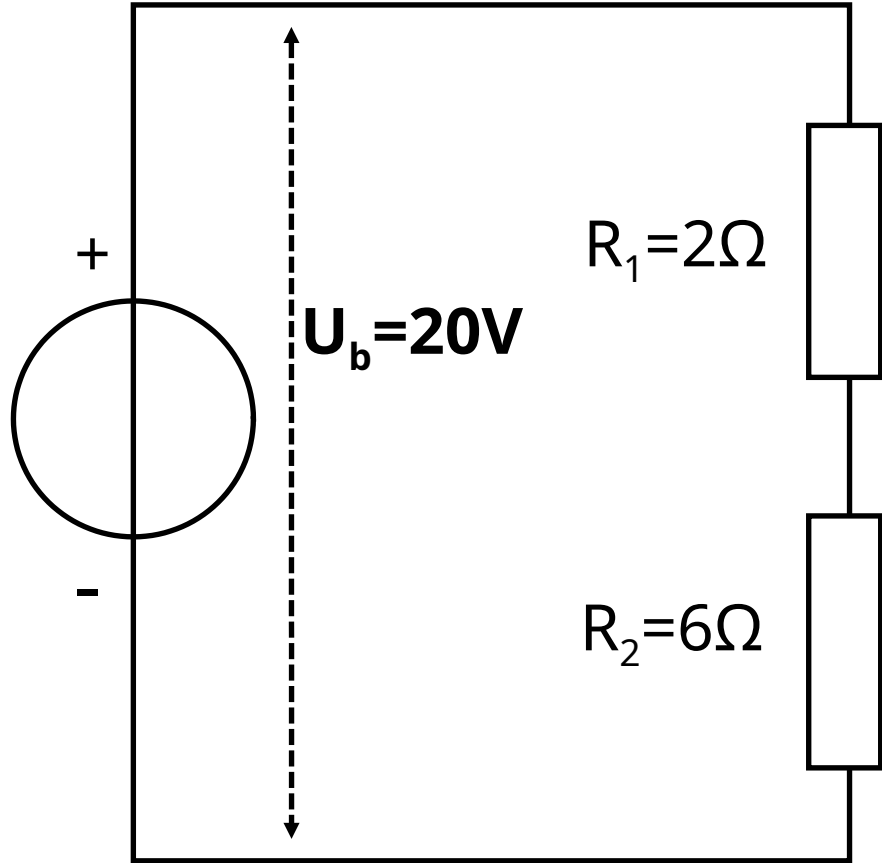

$$U_1 = \frac{R_1}{R_1 + R_2} U_b = \frac{2}{2 + 6} \times 20 \text{ V} = \mathbf{5V}$$

$$U_2 = \frac{R_2}{R_1 + R_2} U_b = \frac{6}{2 + 6} \times 20 \text{ V} = \mathbf{15V}$$

Spanningsdeler

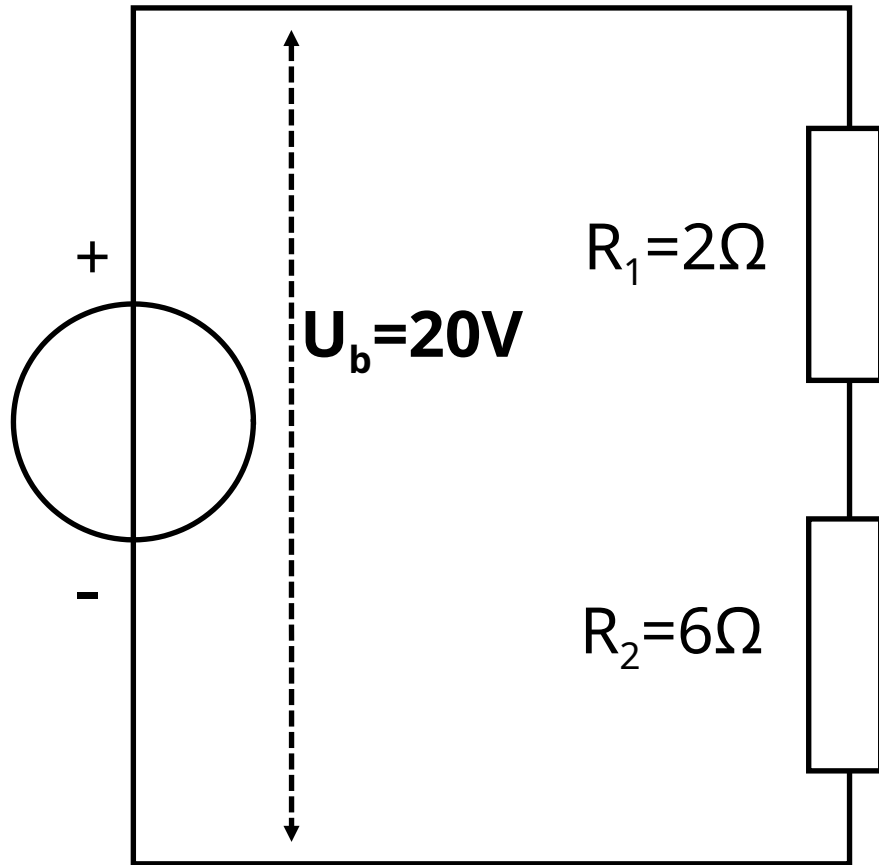


$$U_1 = \frac{R_1}{R_1 + R_2} U_b = \frac{2}{2+6} \times 20 \text{ V} = \mathbf{5V}$$

$$U_2 = \frac{R_2}{R_1 + R_2} U_b = \frac{6}{2+6} \times 20 \text{ V} = \mathbf{15V}$$


$$I = \frac{15V}{6\Omega} = 2\frac{1}{2} \text{ A}$$

Spanningsdeler

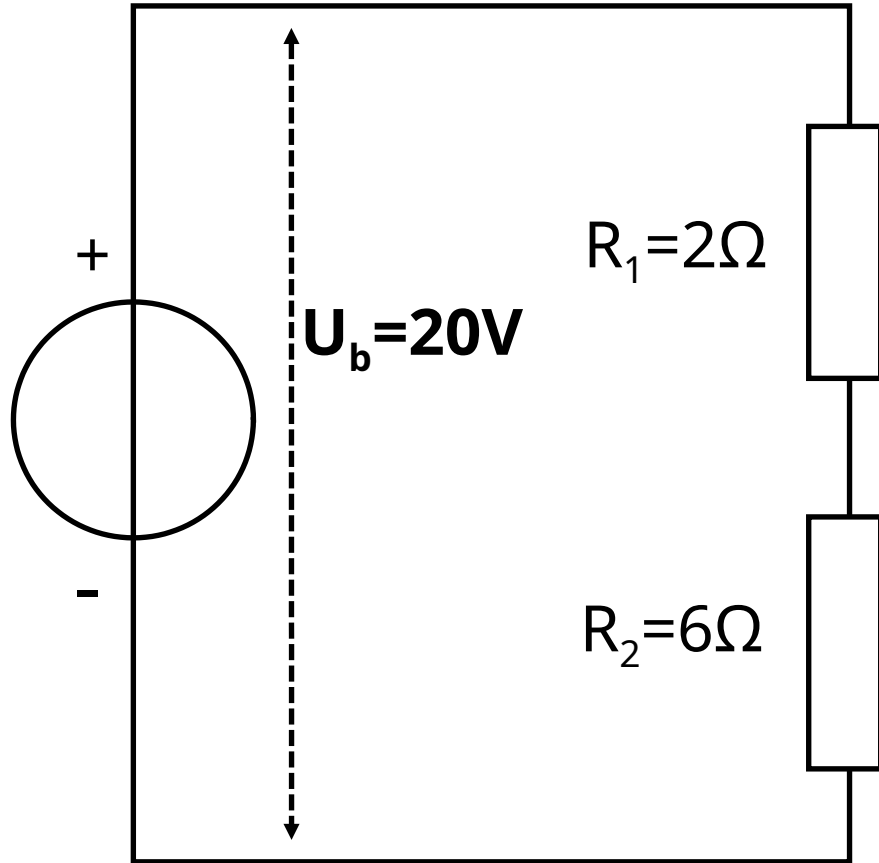

$$U_1 = \frac{R_1}{R_1 + R_2} U_b = \frac{2}{2 + 6} \times 20 \text{ V} = \mathbf{5\text{V}}$$
$$I = \frac{5\text{V}}{2\Omega} = 2\frac{1}{2} \text{ A}$$
$$U_2 = \frac{R_2}{R_1 + R_2} U_b = \frac{6}{2 + 6} \times 20 \text{ V} = \mathbf{15\text{V}}$$
$$I = \frac{15\text{V}}{6\Omega} = 2\frac{1}{2} \text{ A}$$

Spanningsdeler

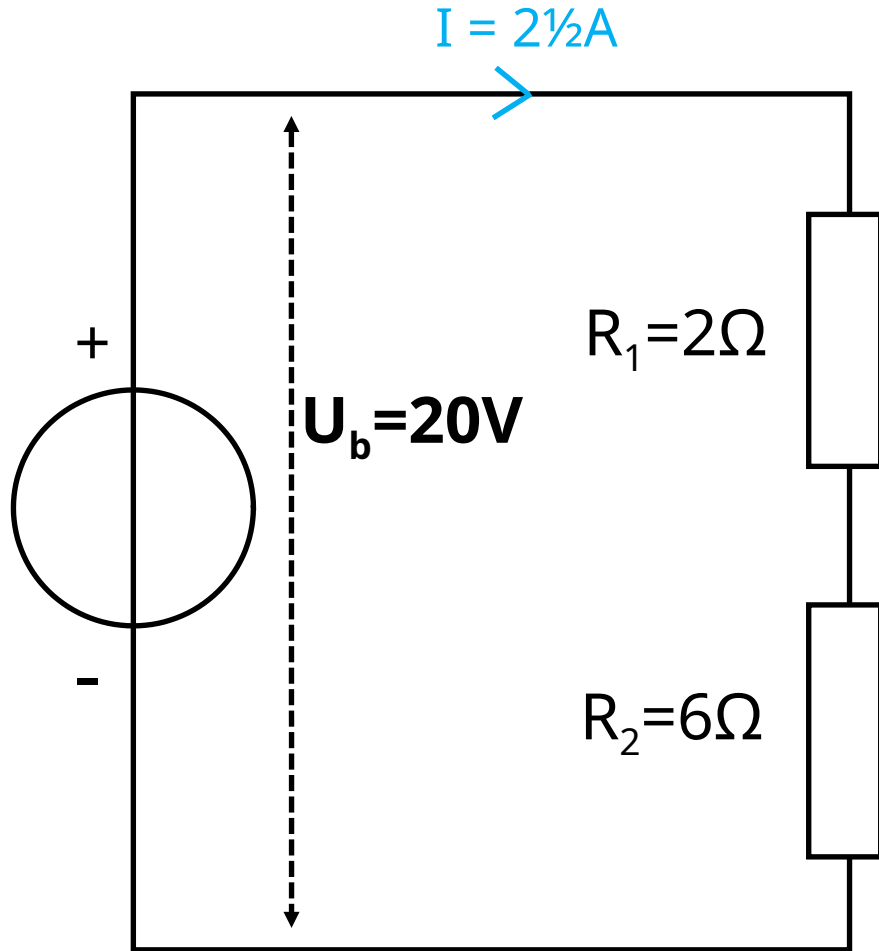


$$U_1 = \frac{R_1}{R_1 + R_2} U_b = \frac{2}{2 + 6} \times 20 \text{ V} = \mathbf{5V}$$

$I = \frac{5V}{2\Omega} = 2\frac{1}{2} A$

$$U_2 = \frac{R_2}{R_1 + R_2} U_b = \frac{6}{2 + 6} \times 20 \text{ V} = \mathbf{15V}$$

$I = \frac{15V}{6\Omega} = 2\frac{1}{2} A$

Spanningsdeler

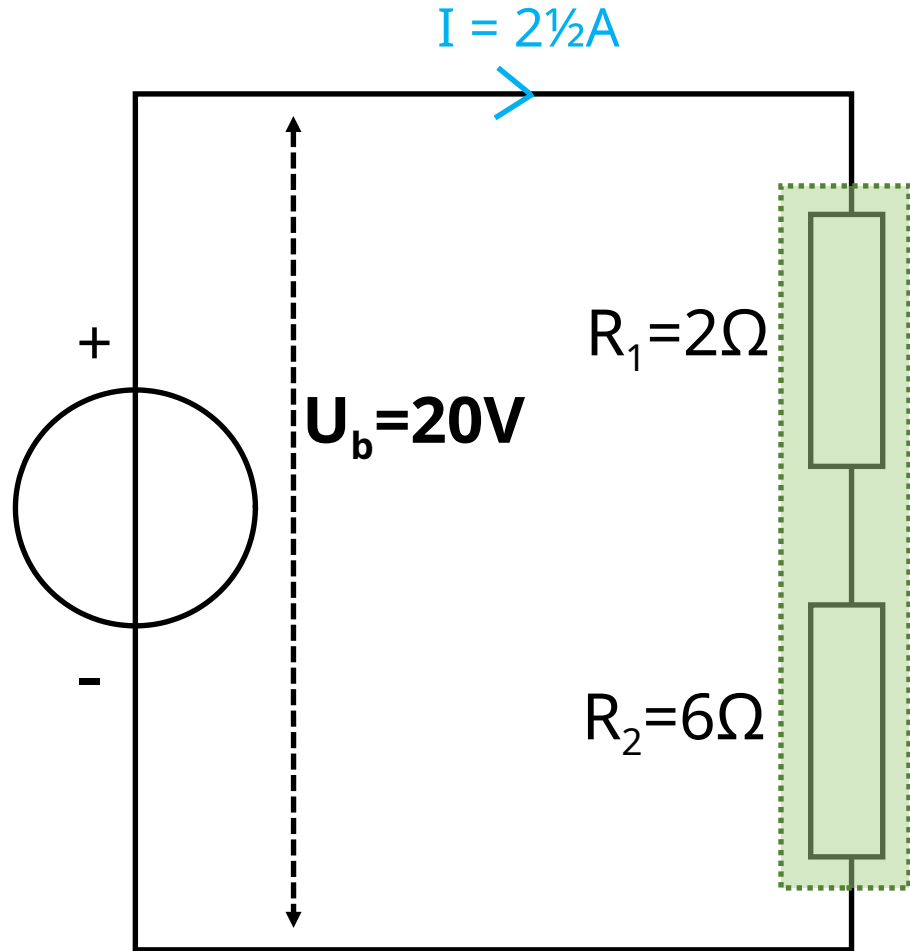

$$U_1 = \frac{R_1}{R_1 + R_2} U_b = \frac{2}{2 + 6} \times 20 \text{ V} = \mathbf{5V}$$


$$I = \frac{5V}{2\Omega} = 2\frac{1}{2} \text{ A}$$

$$U_2 = \frac{R_2}{R_1 + R_2} U_b = \frac{6}{2 + 6} \times 20 \text{ V} = \mathbf{15V}$$

$$I = \frac{15V}{6\Omega} = 2\frac{1}{2} \text{ A}$$

$$R_v = (2 + 6)\Omega = 8\Omega$$

Spanningsdeler

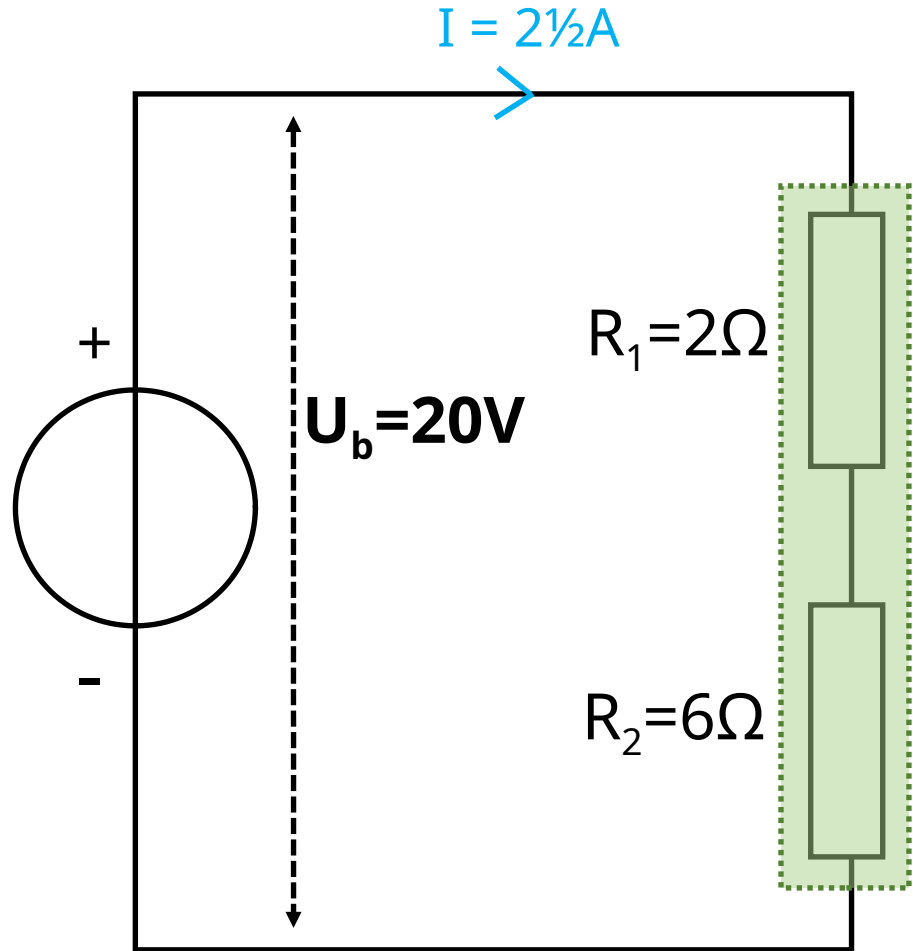

$$U_1 = \frac{R_1}{R_1 + R_2} U_b = \frac{2}{2 + 6} \times 20 \text{ V} = \mathbf{5V}$$

$$I = \frac{5V}{2\Omega} = 2\frac{1}{2} \text{ A}$$


$$U_2 = \frac{R_2}{R_1 + R_2} U_b = \frac{6}{2 + 6} \times 20 \text{ V} = \mathbf{15V}$$

$$I = \frac{15V}{6\Omega} = 2\frac{1}{2} \text{ A}$$


$$R_v = (2 + 6)\Omega = 8\Omega$$

$$\text{Check: } U_b = R_v \times I = 8\Omega \times 2\frac{1}{2}A = 20V$$

Stroomdeler

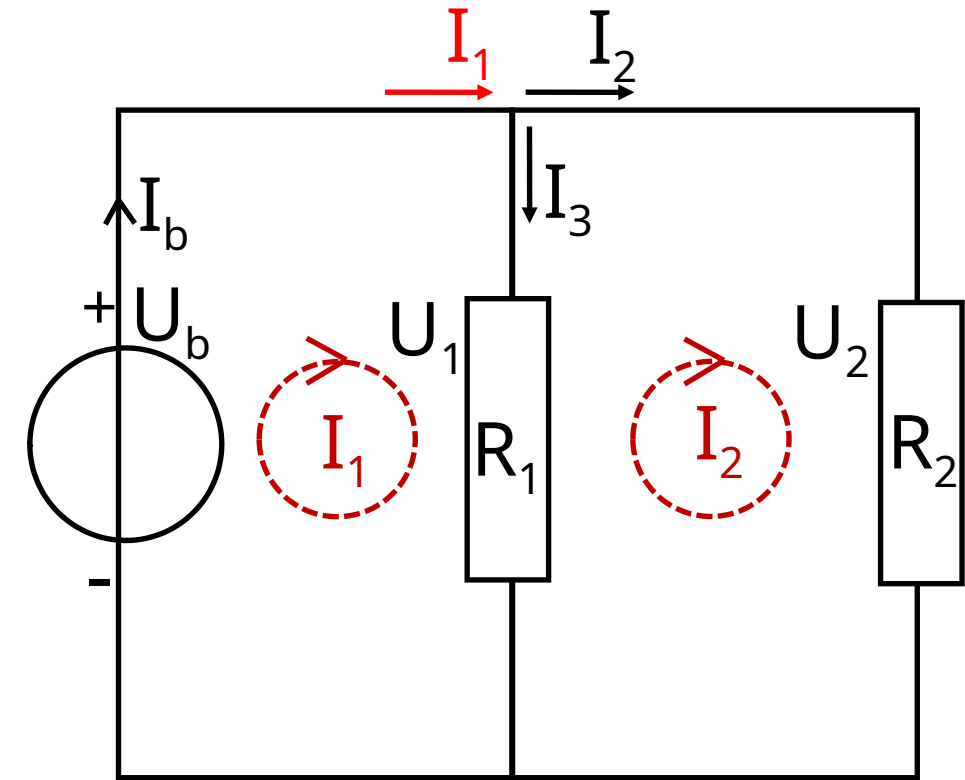


Stromdeler

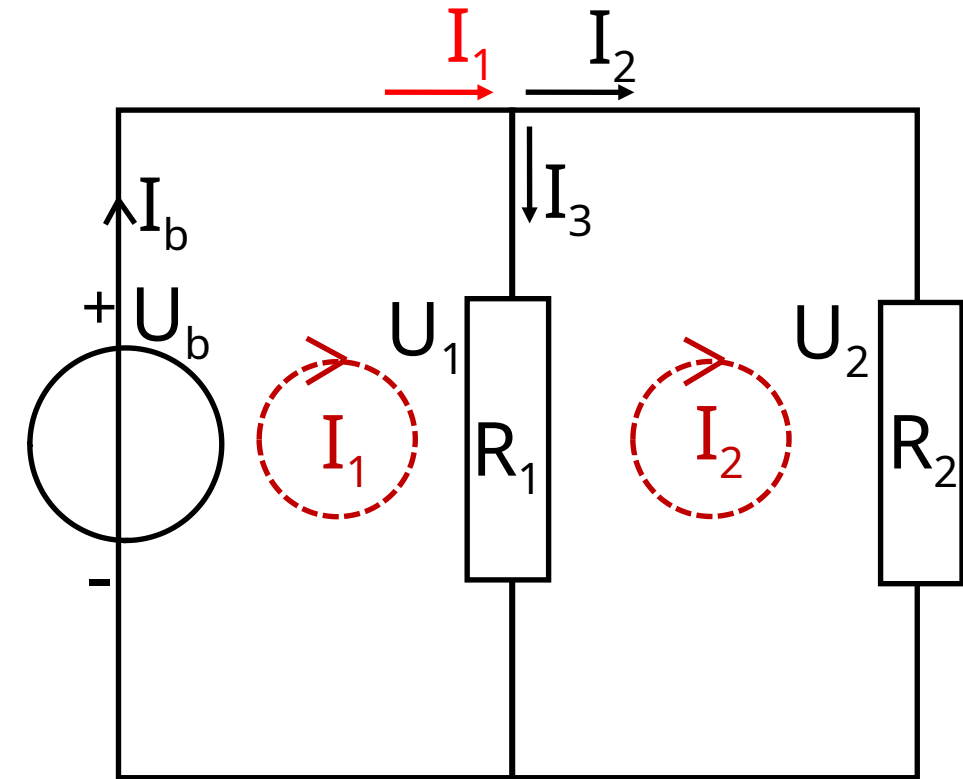

K2: $U_b + -U_1 = 0 \Rightarrow U_b = U_1$


Stromdeler

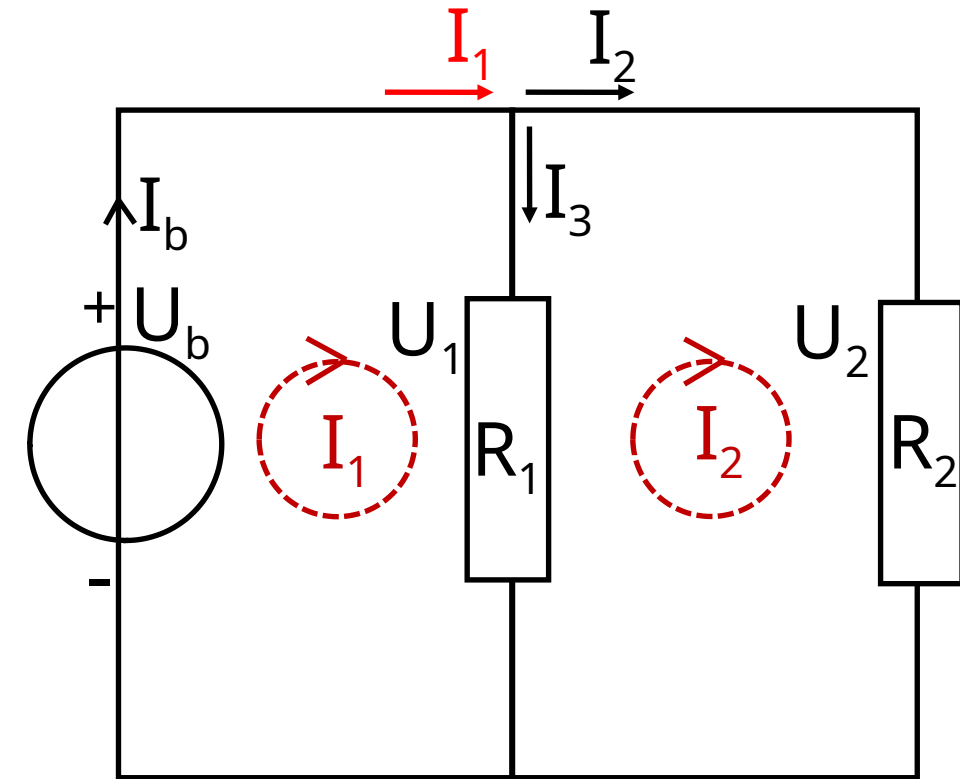

K2:

$$U_b + -U_1 = 0 \quad \Rightarrow \quad U_b = U_1$$
$$U_1 + -U_2 = 0 \quad \Rightarrow \quad 0 = -U_1 + U_2$$


Stromdeler

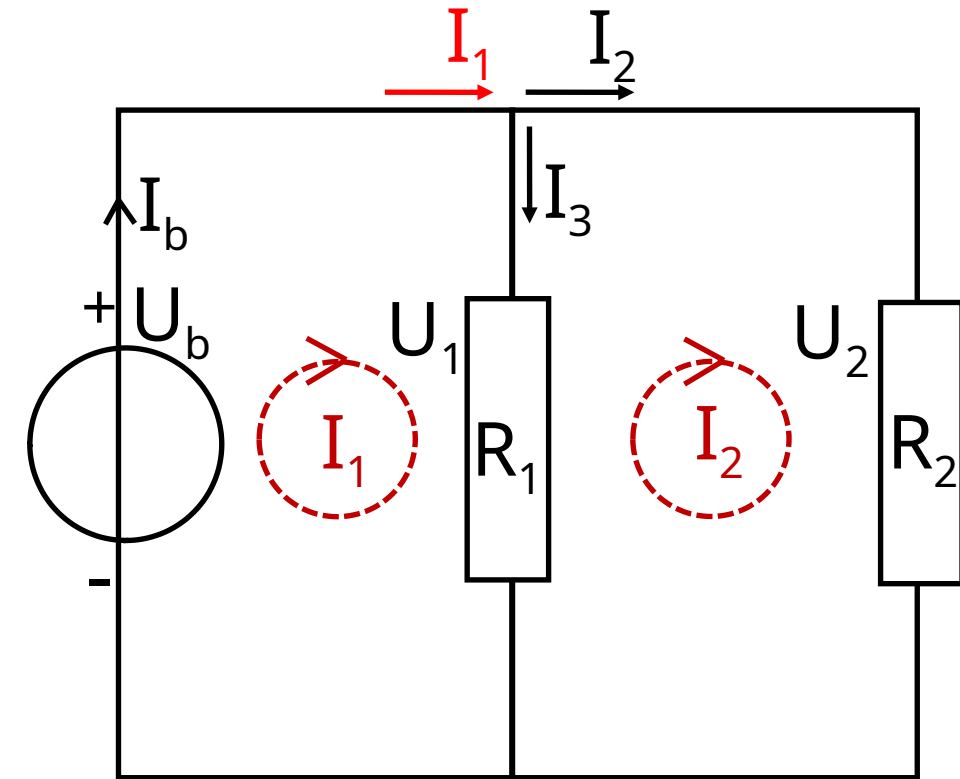

K2: $U_b + -U_1 = 0 \Rightarrow U_b = U_1$
 $U_1 + -U_2 = 0 \Rightarrow 0 = -U_1 + U_2$

Ohm: $U_b = R_1 I_3 \Rightarrow U_b = R_1 I_1 - R_1 I_2$
 $= R_1 (I_1 - I_2)$

Stromdeler

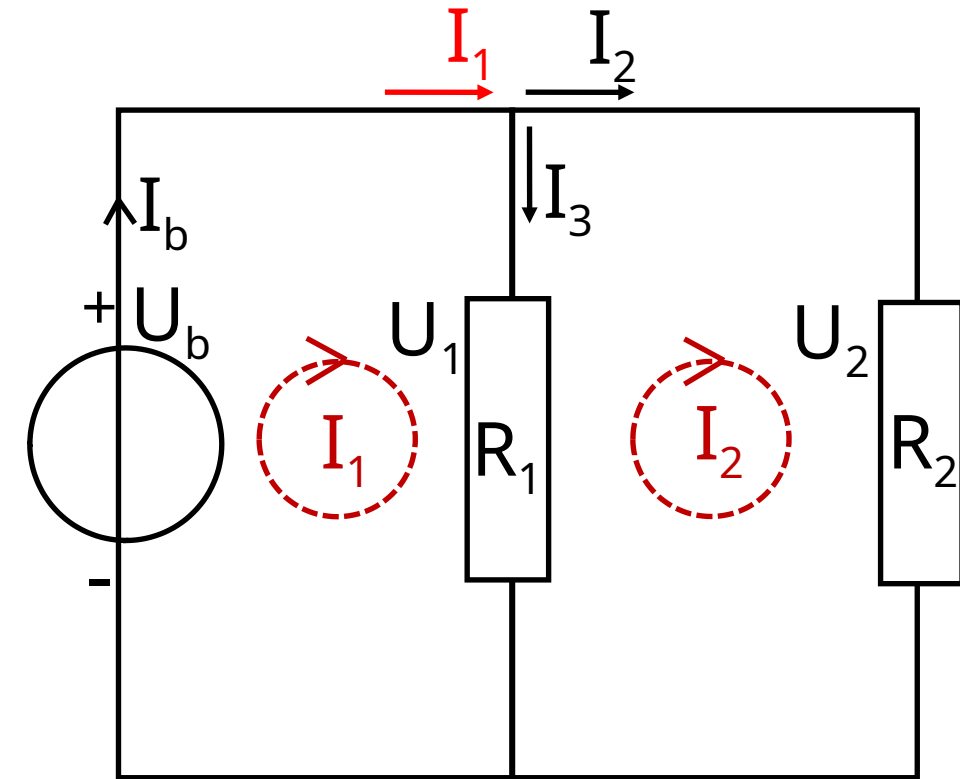


K2: $U_b + -U_1 = 0 \Rightarrow U_b = U_1$

$U_1 + -U_2 = 0 \Rightarrow 0 = -U_1 + U_2$

Ohm: $U_b = R_1 I_3 \Rightarrow U_b = R_1 I_1 - R_1 I_2$
 $= R_1 (I_1 - I_2)$

$0 = -R_1 I_3 + R_2 I_2 \Rightarrow 0 = -R_1 I_1 + (R_1 + R_2) I_2$
 $= -R_1 (I_1 - I_2) + R_2 I_2 = -R_1 I_1 + R_1 I_2 + R_2 I_2$

Stromdeler

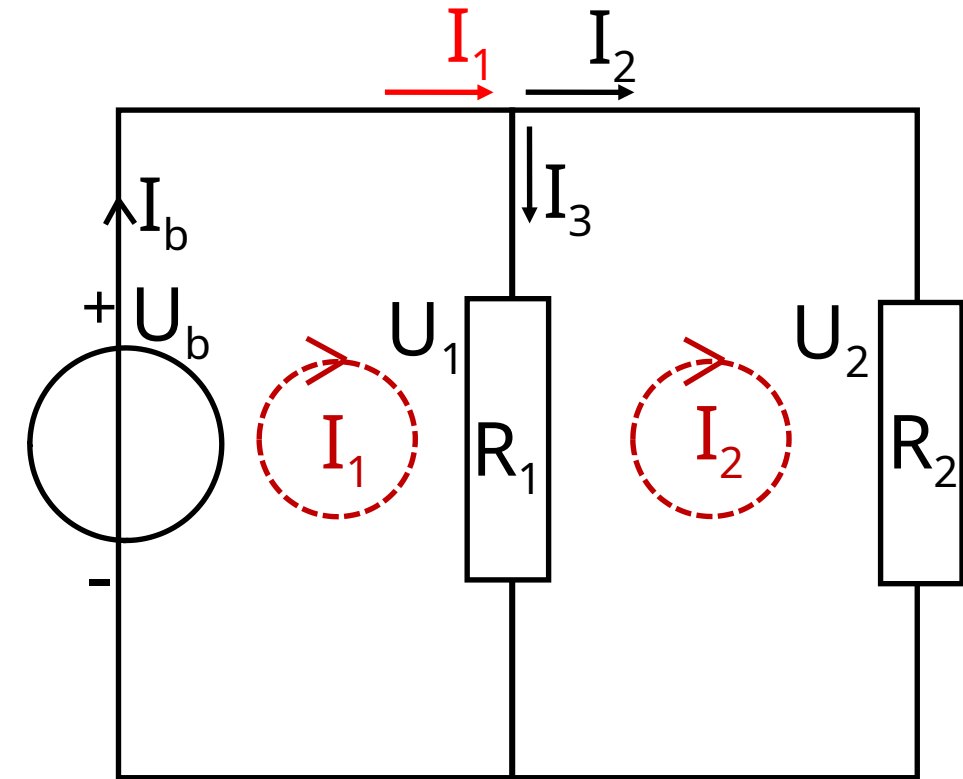

K2: $U_b + -U_1 = 0 \Rightarrow U_b = U_1$

$U_1 + -U_2 = 0 \Rightarrow 0 = -U_1 + U_2$

Ohm: $U_b = R_1 I_3 \Rightarrow U_b = R_1 I_1 - R_1 I_2$


$= R_1 (I_1 - I_2)$

$0 = -R_1 I_3 + R_2 I_2 \Rightarrow 0 = -R_1 I_1 + (R_1 + R_2) I_2$

$= -R_1 (I_1 - I_2) + R_2 I_2 = -R_1 I_1 + R_1 I_2 + R_2 I_2$

$$\begin{pmatrix} U_b \\ 0 \end{pmatrix} = \begin{pmatrix} R_1 & -R_1 \\ -R_1 & R_1 + R_2 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \Rightarrow \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ \frac{1}{R_2} & \frac{1}{R_2} \end{pmatrix} \begin{pmatrix} U_b \\ 0 \end{pmatrix}$$

Stromdeler

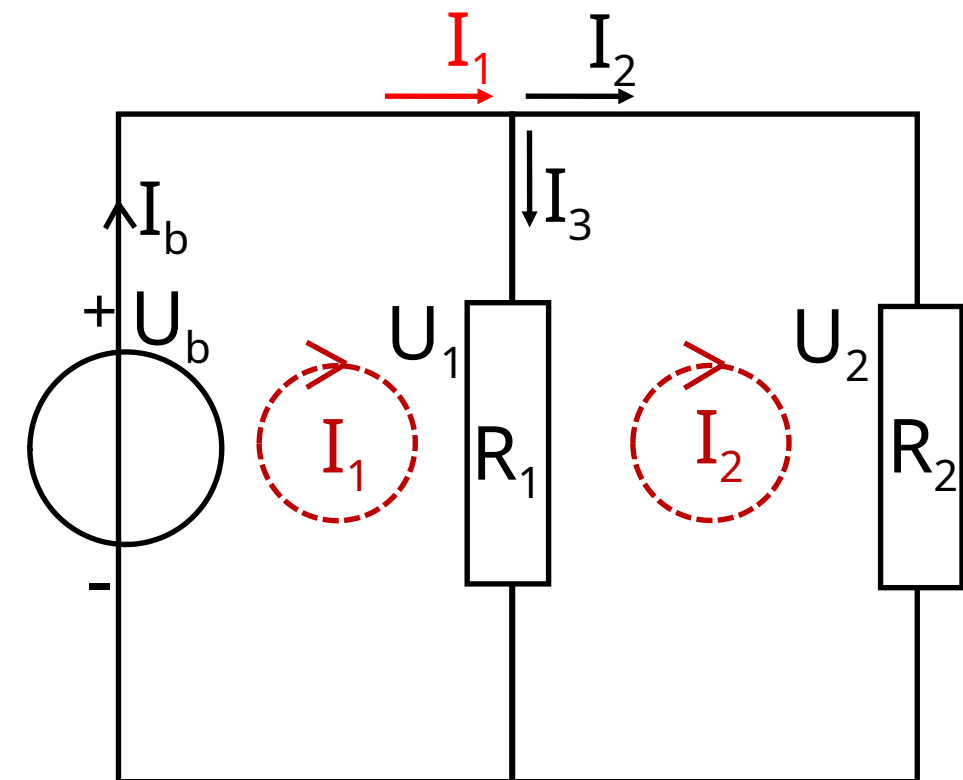


K2: $U_b + -U_1 = 0 \Rightarrow U_b = U_1$
 $U_1 + -U_2 = 0 \Rightarrow 0 = -U_1 + U_2$

Ohm: $U_b = R_1 I_3 \Rightarrow U_b = R_1 I_1 - R_1 I_2$
 $= R_1 (I_1 - I_2)$
 $0 = -R_1 I_3 + R_2 I_2 \Rightarrow 0 = -R_1 I_1 + (R_1 + R_2) I_2$
 $= -R_1 (I_1 - I_2) + R_2 I_2 = -R_1 I_1 + R_1 I_2 + R_2 I_2$

$$\begin{pmatrix} U_b \\ 0 \end{pmatrix} = \begin{pmatrix} R_1 & -R_1 \\ -R_1 & R_1 + R_2 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \Rightarrow \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ \frac{1}{R_2} & \frac{1}{R_2} \end{pmatrix} \begin{pmatrix} U_b \\ 0 \end{pmatrix}$$

$$\left(\begin{array}{cc|cc} R_1 & -R_1 & 1 & 0 \\ -R_1 & R_1 + R_2 & 0 & 1 \end{array} \right) \rightsquigarrow \left(\begin{array}{cc|cc} R_1 & -R_1 & 1 & 0 \\ 0 & R_2 & 1 & 1 \end{array} \right) \rightsquigarrow \left(\begin{array}{cc|cc} 1 & -1 & \frac{1}{R_1} & 0 \\ 0 & 1 & \frac{1}{R_2} & \frac{1}{R_2} \end{array} \right) \rightsquigarrow \left(\begin{array}{cc|cc} 1 & 0 & \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ 0 & 1 & \frac{1}{R_2} & \frac{1}{R_2} \end{array} \right)$$

Stromdeler

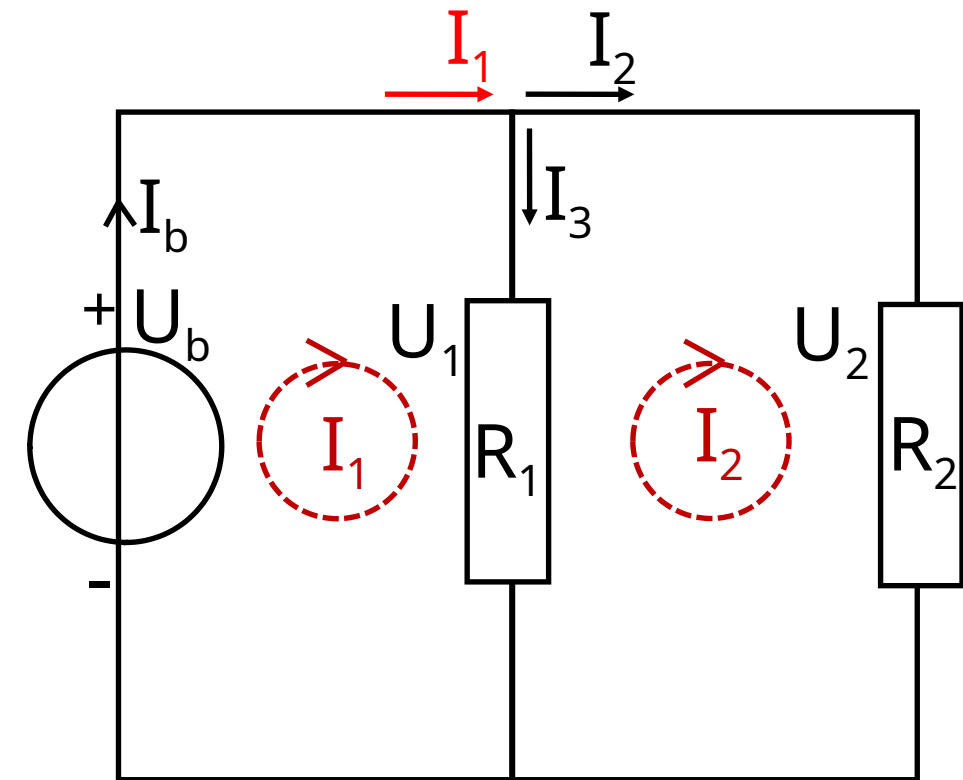

$$\begin{aligned} \text{K2: } U_b + -U_1 &= 0 & \Rightarrow & U_b = U_1 \\ U_1 + -U_2 &= 0 & \Rightarrow & 0 = -U_1 + U_2 \end{aligned}$$


$$\begin{aligned} \text{Ohm: } U_b &= R_1 I_3 & \Rightarrow & U_b = R_1 I_1 - R_1 I_2 \\ &= R_1 (I_1 - I_2) \\ 0 &= -R_1 I_3 + R_2 I_2 & \Rightarrow & 0 = -R_1 I_1 + (R_1 + R_2) I_2 \\ &= -R_1 (I_1 - I_2) + R_2 I_2 = -R_1 I_1 + R_1 I_2 + R_2 I_2 \end{aligned}$$

$$\begin{pmatrix} U_b \\ 0 \end{pmatrix} = \begin{pmatrix} R_1 & -R_1 \\ -R_1 & R_1 + R_2 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \Rightarrow \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ \frac{1}{R_2} & \frac{1}{R_2} \end{pmatrix} \begin{pmatrix} U_b \\ 0 \end{pmatrix}$$

$$\left(\begin{array}{cc|cc} R_1 & -R_1 & 1 & 0 \\ -R_1 & R_1 + R_2 & 0 & 1 \end{array} \right) \rightsquigarrow \left(\begin{array}{cc|cc} R_1 & -R_1 & 1 & 0 \\ 0 & R_2 & 1 & 1 \end{array} \right) \rightsquigarrow \left(\begin{array}{cc|cc} 1 & -1 & \frac{1}{R_1} & 0 \\ 0 & 1 & \frac{1}{R_2} & \frac{1}{R_2} \end{array} \right) \rightsquigarrow \left(\begin{array}{cc|cc} 1 & 0 & \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ 0 & 1 & \frac{1}{R_2} & \frac{1}{R_2} \end{array} \right)$$

$$I_b = I_1 = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) U_b = \left(\frac{R_2}{R_1 R_2} + \frac{R_1}{R_1 R_2} \right) U_b = \frac{R_1 + R_2}{R_1 R_2} U_b \quad \left| \frac{R_1 R_2}{R_1 + R_2} \right. \Rightarrow U_b = \frac{R_1 R_2}{R_1 + R_2} I_b$$

Stromdeler

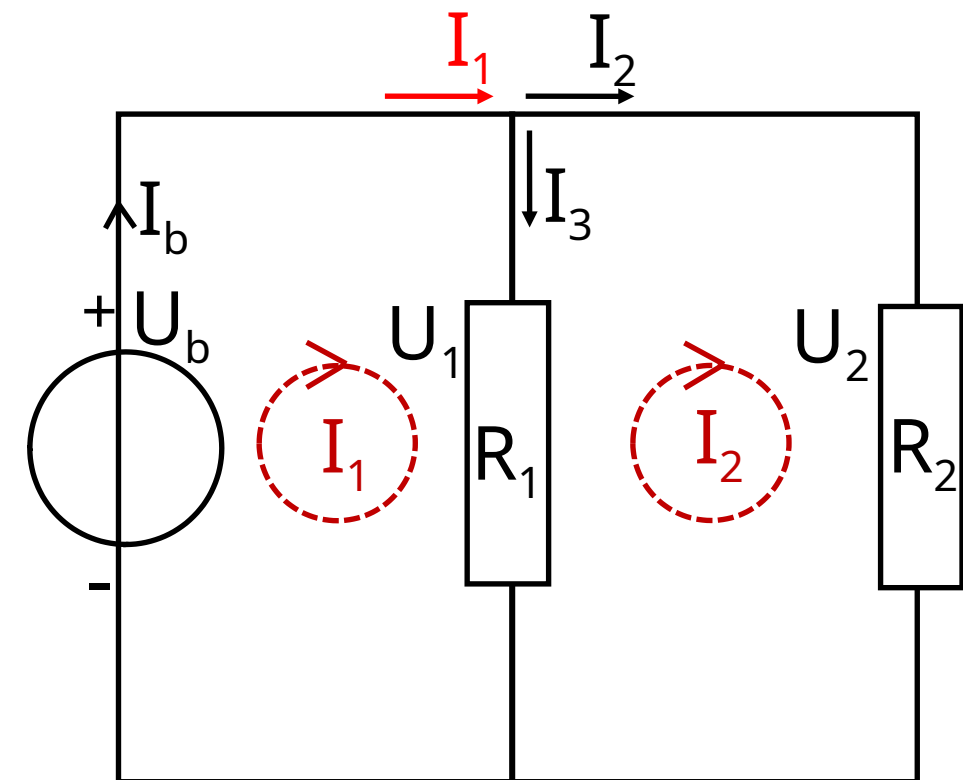

$$\begin{aligned} \text{K2: } U_b + -U_1 &= 0 & \Rightarrow & U_b = U_1 \\ U_1 + -U_2 &= 0 & \Rightarrow & 0 = -U_1 + U_2 \end{aligned}$$

$$\begin{aligned} \text{Ohm: } U_b &= R_1 I_3 & \Rightarrow & U_b = R_1 I_1 - R_1 I_2 \\ &= R_1 (I_1 - I_2) \\ 0 &= -R_1 I_3 + R_2 I_2 & \Rightarrow & 0 = -R_1 I_1 + (R_1 + R_2) I_2 \\ &= -R_1 (I_1 - I_2) + R_2 I_2 = -R_1 I_1 + R_1 I_2 + R_2 I_2 \end{aligned}$$


$$\begin{pmatrix} U_b \\ 0 \end{pmatrix} = \begin{pmatrix} R_1 & -R_1 \\ -R_1 & R_1 + R_2 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \Rightarrow \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ \frac{1}{R_2} & \frac{1}{R_2} \end{pmatrix} \begin{pmatrix} U_b \\ 0 \end{pmatrix}$$

$$\left(\begin{array}{cc|cc} R_1 & -R_1 & 1 & 0 \\ -R_1 & R_1 + R_2 & 0 & 1 \end{array} \right) \rightsquigarrow \left(\begin{array}{cc|cc} R_1 & -R_1 & 1 & 0 \\ 0 & R_2 & 1 & 1 \end{array} \right) \rightsquigarrow \left(\begin{array}{cc|cc} 1 & -1 & \frac{1}{R_1} & 0 \\ 0 & 1 & \frac{1}{R_2} & \frac{1}{R_2} \end{array} \right) \rightsquigarrow \left(\begin{array}{cc|cc} 1 & 0 & \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ 0 & 1 & \frac{1}{R_2} & \frac{1}{R_2} \end{array} \right)$$

$$I_b = I_1 = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) U_b = \left(\frac{R_2}{R_1 R_2} + \frac{R_1}{R_1 R_2} \right) U_b = \frac{R_1 + R_2}{R_1 R_2} U_b \quad \left| \frac{R_1 R_2}{R_1 + R_2} \right. \Rightarrow U_b = \frac{R_1 R_2}{R_1 + R_2} I_b$$

$$G_v = G_1 + G_2$$

Stromdeler

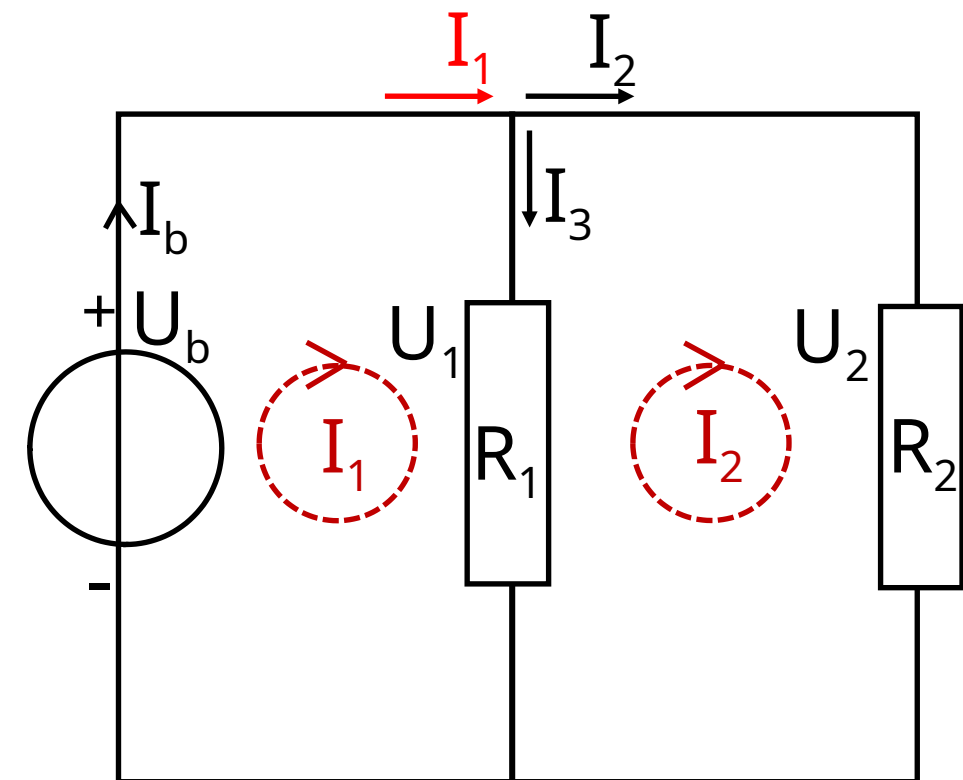

$$\begin{aligned} \text{K2: } U_b + -U_1 &= 0 & \Rightarrow & U_b = U_1 \\ U_1 + -U_2 &= 0 & \Rightarrow & 0 = -U_1 + U_2 \end{aligned}$$

$$\begin{aligned} \text{Ohm: } U_b &= R_1 I_3 & \Rightarrow & U_b = R_1 I_1 - R_1 I_2 \\ &= R_1 (I_1 - I_2) \\ 0 &= -R_1 I_3 + R_2 I_2 & \Rightarrow & 0 = -R_1 I_1 + (R_1 + R_2) I_2 \\ &= -R_1 (I_1 - I_2) + R_2 I_2 = -R_1 I_1 + R_1 I_2 + R_2 I_2 \end{aligned}$$


$$\begin{pmatrix} U_b \\ 0 \end{pmatrix} = \begin{pmatrix} R_1 & -R_1 \\ -R_1 & R_1 + R_2 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \Rightarrow \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ \frac{1}{R_2} & \frac{1}{R_2} \end{pmatrix} \begin{pmatrix} U_b \\ 0 \end{pmatrix}$$

$$\left(\begin{array}{cc|cc} R_1 & -R_1 & 1 & 0 \\ -R_1 & R_1 + R_2 & 0 & 1 \end{array} \right) \rightarrow \left(\begin{array}{cc|cc} R_1 & -R_1 & 1 & 0 \\ 0 & R_2 & 1 & 1 \end{array} \right) \rightarrow \left(\begin{array}{cc|cc} 1 & -1 & \frac{1}{R_1} & 0 \\ 0 & 1 & \frac{1}{R_2} & \frac{1}{R_2} \end{array} \right) \rightarrow \left(\begin{array}{cc|cc} 1 & 0 & \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ 0 & 1 & \frac{1}{R_2} & \frac{1}{R_2} \end{array} \right)$$

$$I_b = I_1 = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) U_b = \left(\frac{R_2}{R_1 R_2} + \frac{R_1}{R_1 R_2} \right) U_b = \frac{R_1 + R_2}{R_1 R_2} U_b \quad \left| \frac{R_1 R_2}{R_1 + R_2} \right. \Rightarrow U_b = \frac{R_1 R_2}{R_1 + R_2} I_b$$

$G_v = G_1 + G_2$ R_v

Stromdeler

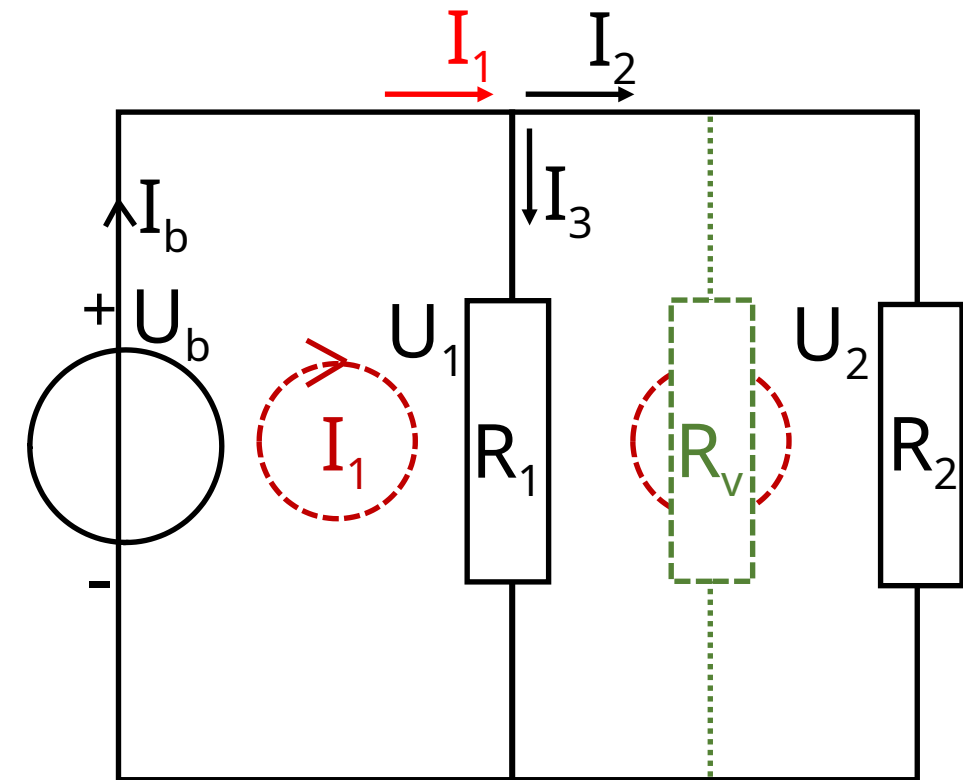

K2: $U_b + -U_1 = 0 \Rightarrow U_b = U_1$
 $U_1 + -U_2 = 0 \Rightarrow 0 = -U_1 + U_2$


Ohm: $U_b = R_1 I_3 \Rightarrow U_b = R_1 I_1 - R_1 I_2$
 $= R_1 (I_1 - I_2)$
 $0 = -R_1 I_3 + R_2 I_2 \Rightarrow 0 = -R_1 I_1 + (R_1 + R_2) I_2$
 $= -R_1 (I_1 - I_2) + R_2 I_2 = -R_1 I_1 + R_1 I_2 + R_2 I_2$


$$\begin{pmatrix} U_b \\ 0 \end{pmatrix} = \begin{pmatrix} R_1 & -R_1 \\ -R_1 & R_1 + R_2 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} \Rightarrow \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ \frac{1}{R_2} & \frac{1}{R_2} \end{pmatrix} \begin{pmatrix} U_b \\ 0 \end{pmatrix}$$


$$\left(\begin{array}{cc|cc} R_1 & -R_1 & 1 & 0 \\ -R_1 & R_1 + R_2 & 0 & 1 \end{array} \right) \rightarrow \left(\begin{array}{cc|cc} R_1 & -R_1 & 1 & 0 \\ 0 & R_2 & 1 & 1 \end{array} \right) \rightarrow \left(\begin{array}{cc|cc} 1 & -1 & \frac{1}{R_1} & 0 \\ 0 & 1 & \frac{1}{R_2} & \frac{1}{R_2} \end{array} \right) \rightarrow \left(\begin{array}{cc|cc} 1 & 0 & \frac{1}{R_1} + \frac{1}{R_2} & \frac{1}{R_2} \\ 0 & 1 & \frac{1}{R_2} & \frac{1}{R_2} \end{array} \right)$$

$$I_b = I_1 = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) U_b = \left(\frac{R_2}{R_1 R_2} + \frac{R_1}{R_1 R_2} \right) U_b = \frac{R_1 + R_2}{R_1 R_2} U_b \quad \left| \frac{R_1 R_2}{R_1 + R_2} \right. \Rightarrow U_b = \frac{R_1 R_2}{R_1 + R_2} I_b$$


$G_v = G_1 + G_2$ R_v

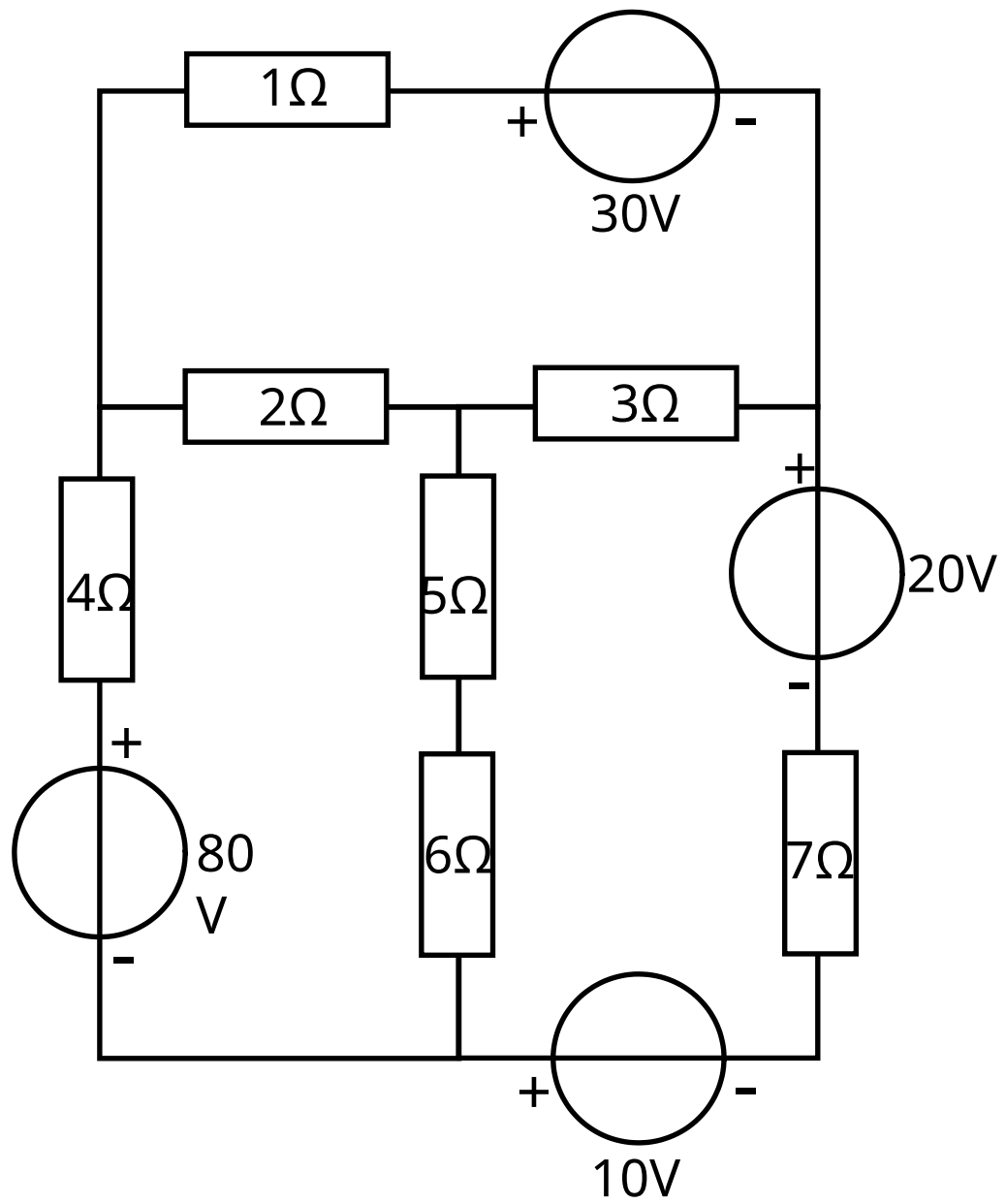

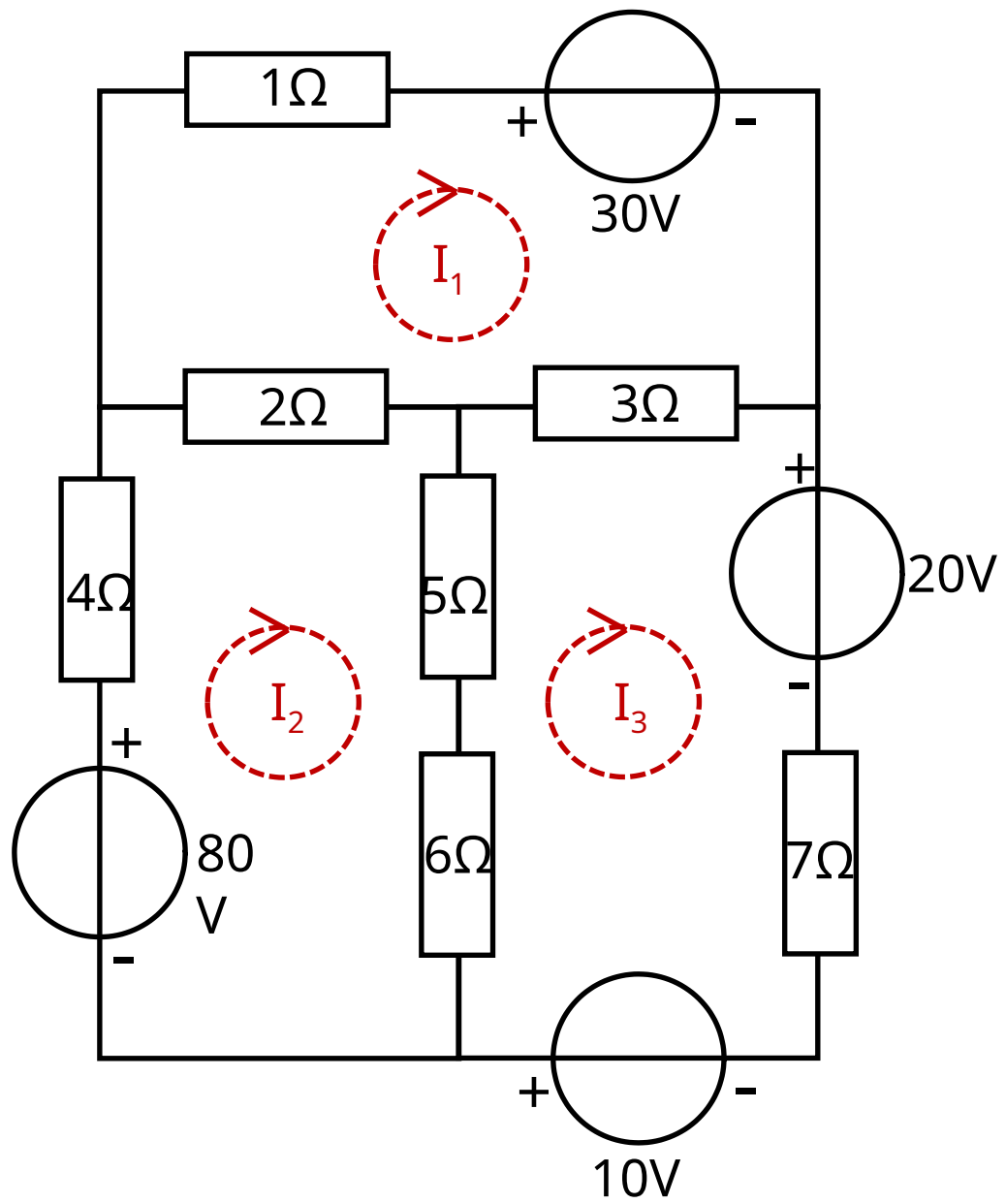

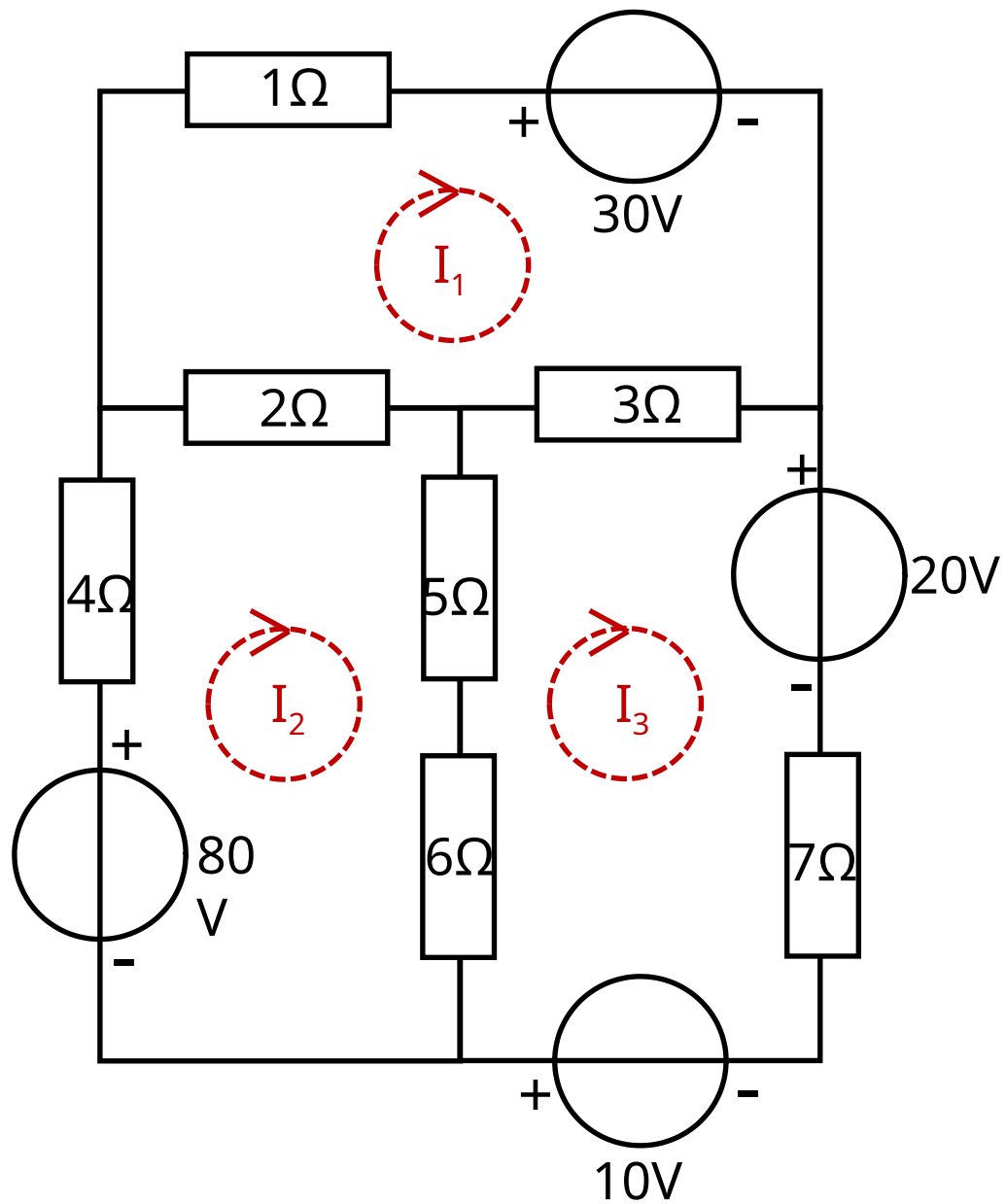

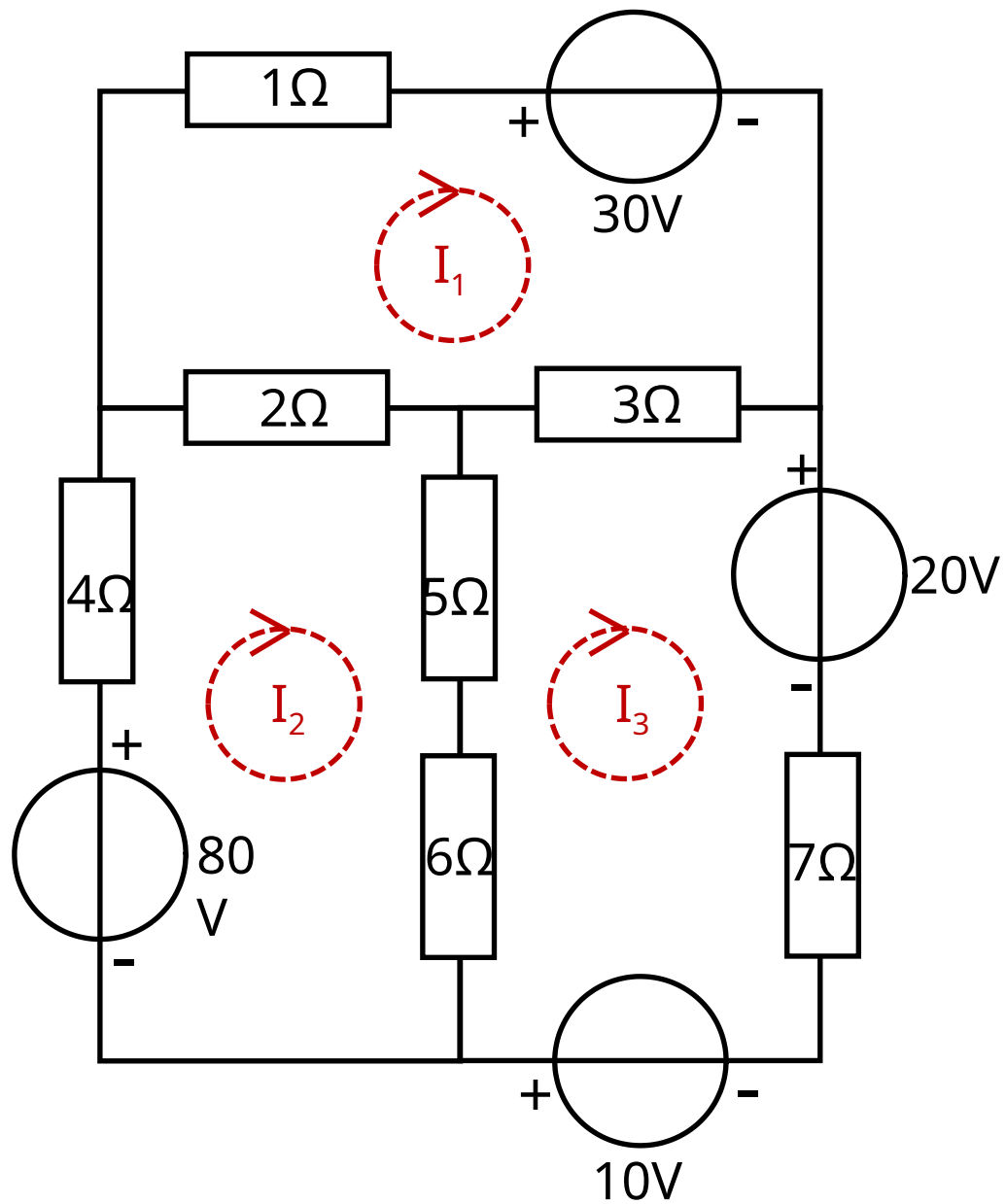
$$\begin{aligned}
 -30 &= (1+3+2) I_1 + -2 I_2 + -3 I_3 \\
 80 &= -2 I_1 + (2+5+6+4) I_2 + (-5-6) I_3 \\
 -20 + 10 &= -3 I_1 + (-6-5) I_2 + (3+7+6+5) I_3
 \end{aligned}$$



$$\begin{aligned}
 -30 &= (1+3+2) I_1 + -2 I_2 + -3 I_3 \\
 80 &= -2 I_1 + (2+5+6+4) I_2 + (-5-6) I_3 \\
 -20 + 10 &= -3 I_1 + (-6-5) I_2 + (3+7+6+5) I_3
 \end{aligned}$$

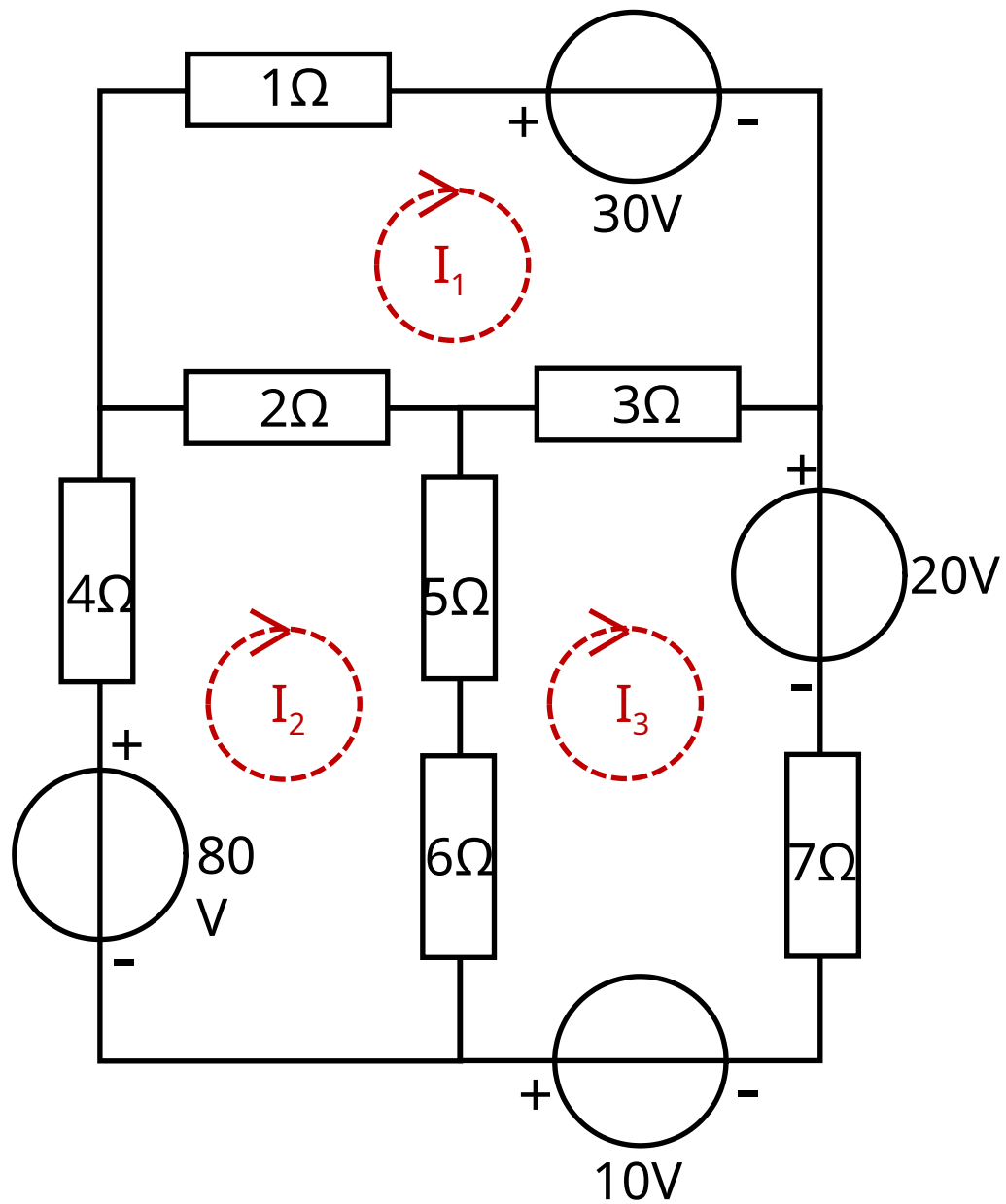
$$\Rightarrow \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$



$$\begin{aligned}
 -30 &= (1+3+2) I_1 + -2 I_2 + -3 I_3 \\
 80 &= -2 I_1 + (2+5+6+4) I_2 + (-5-6) I_3 \\
 -20 + 10 &= -3 I_1 + (-6-5) I_2 + (3+7+6+5) I_3
 \end{aligned}$$

$$\Rightarrow \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$
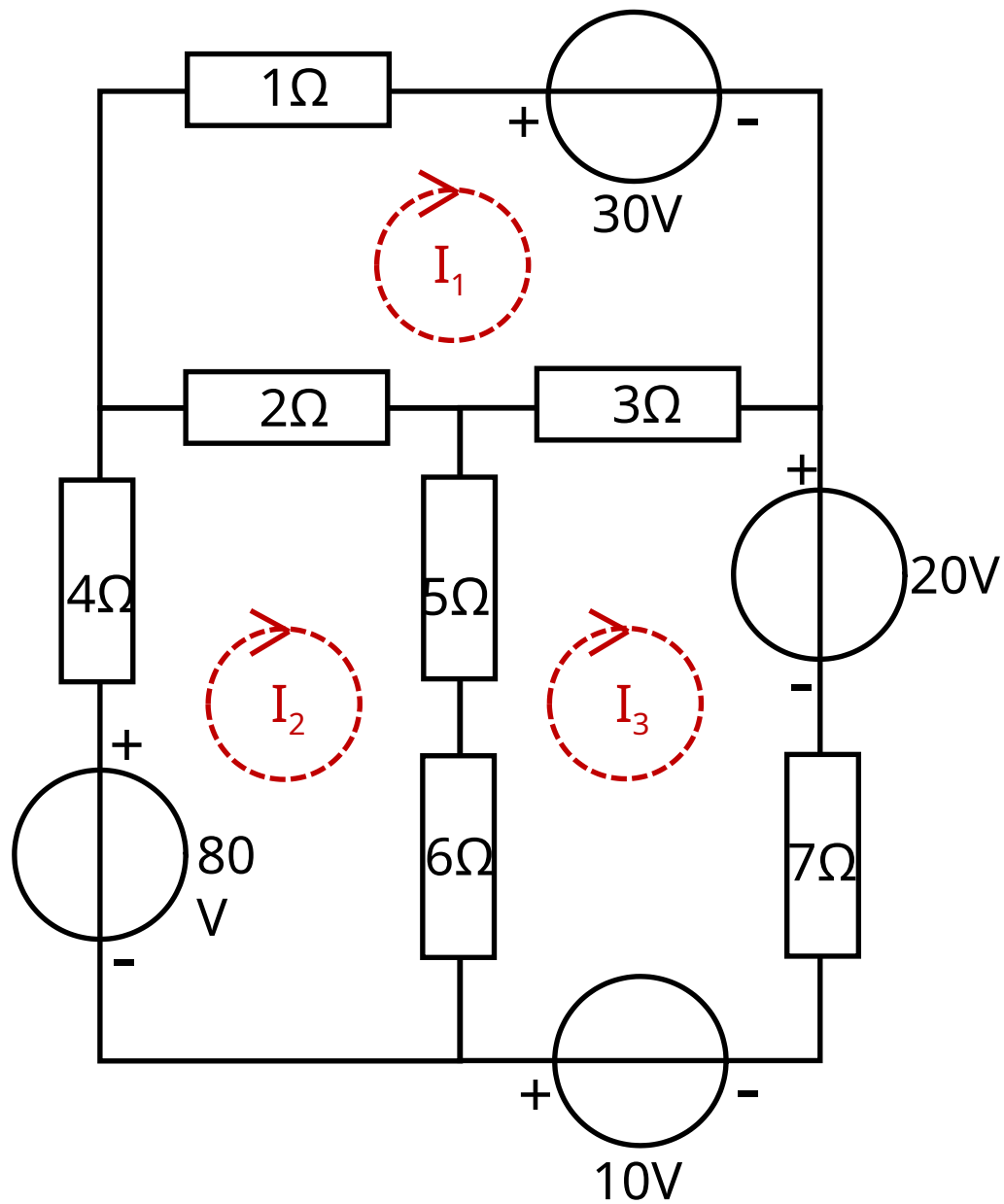
$$\Rightarrow \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix}^{-1} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix}$$




$$\begin{aligned}
 -30 &= (1+3+2) I_1 + -2 I_2 + -3 I_3 \\
 80 &= -2 I_1 + (2+5+6+4) I_2 + (-5-6) I_3 \\
 -20 + 10 &= -3 I_1 + (-6-5) I_2 + (3+7+6+5) I_3
 \end{aligned}$$

$$\Rightarrow \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix}^{-1} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix}$$
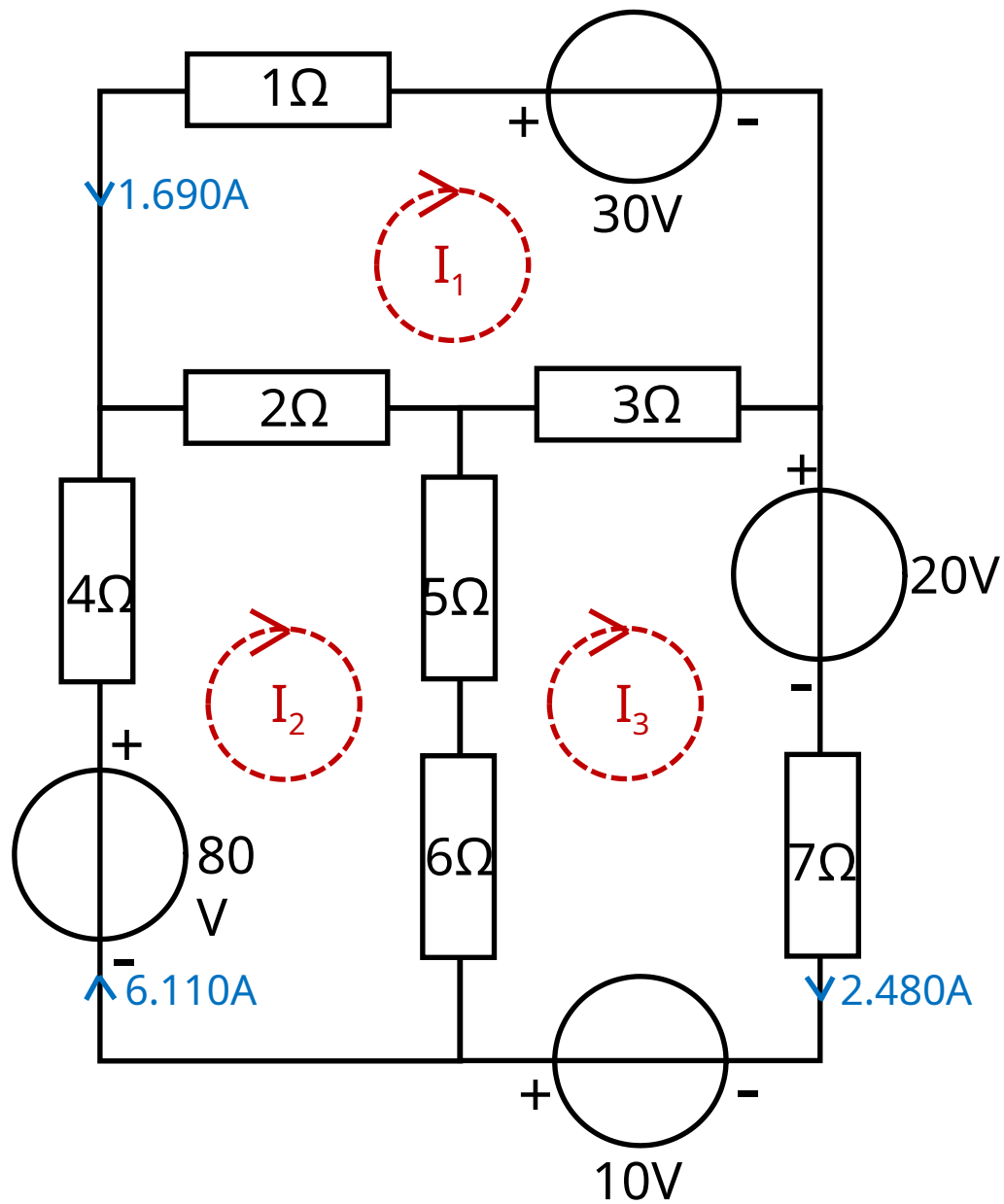
$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0.225 & 0.072 & 0.070 \\ 0.072 & 0.112 & 0.069 \\ 0.070 & 0.069 & 0.094 \end{pmatrix} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} -1.690 \\ 6.110 \\ 2.480 \end{pmatrix} \text{ [A]}$$




$$\begin{aligned}
 -30 &= (1+3+2) I_1 + -2 I_2 + -3 I_3 \\
 80 &= -2 I_1 + (2+5+6+4) I_2 + (-5-6) I_3 \\
 -20 + 10 &= -3 I_1 + (-6-5) I_2 + (3+7+6+5) I_3
 \end{aligned}$$

$$\Rightarrow \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix}^{-1} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix}$$
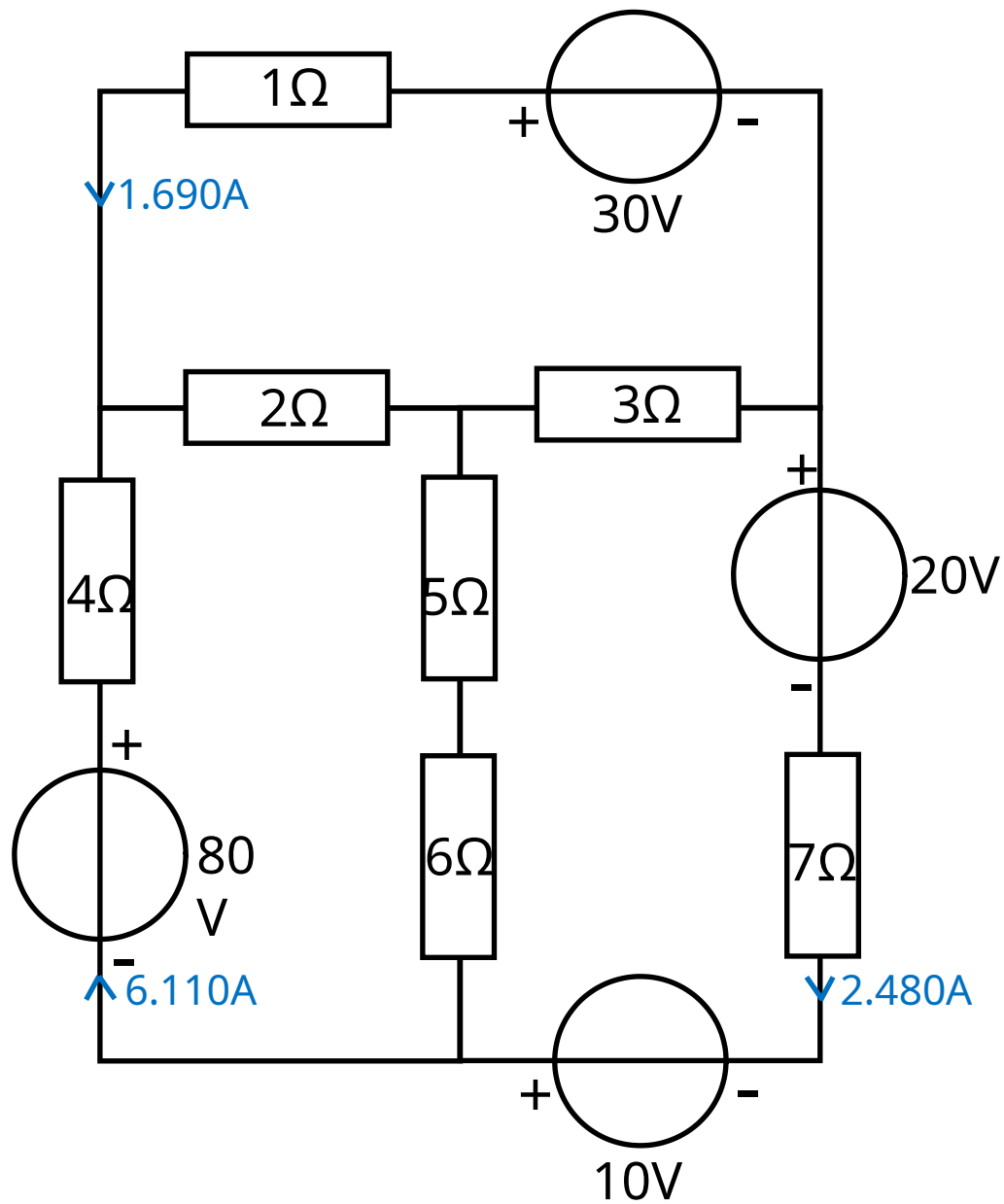
$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0.225 & 0.072 & 0.070 \\ 0.072 & 0.112 & 0.069 \\ 0.070 & 0.069 & 0.094 \end{pmatrix} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} -1.690 \\ 6.110 \\ 2.480 \end{pmatrix} \text{ [A]}$$




$$\begin{aligned}
 -30 &= (1+3+2) I_1 + -2 I_2 + -3 I_3 \\
 80 &= -2 I_1 + (2+5+6+4) I_2 + (-5-6) I_3 \\
 -20 + 10 &= -3 I_1 + (-6-5) I_2 + (3+7+6+5) I_3
 \end{aligned}$$

$$\Rightarrow \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix}^{-1} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix}$$
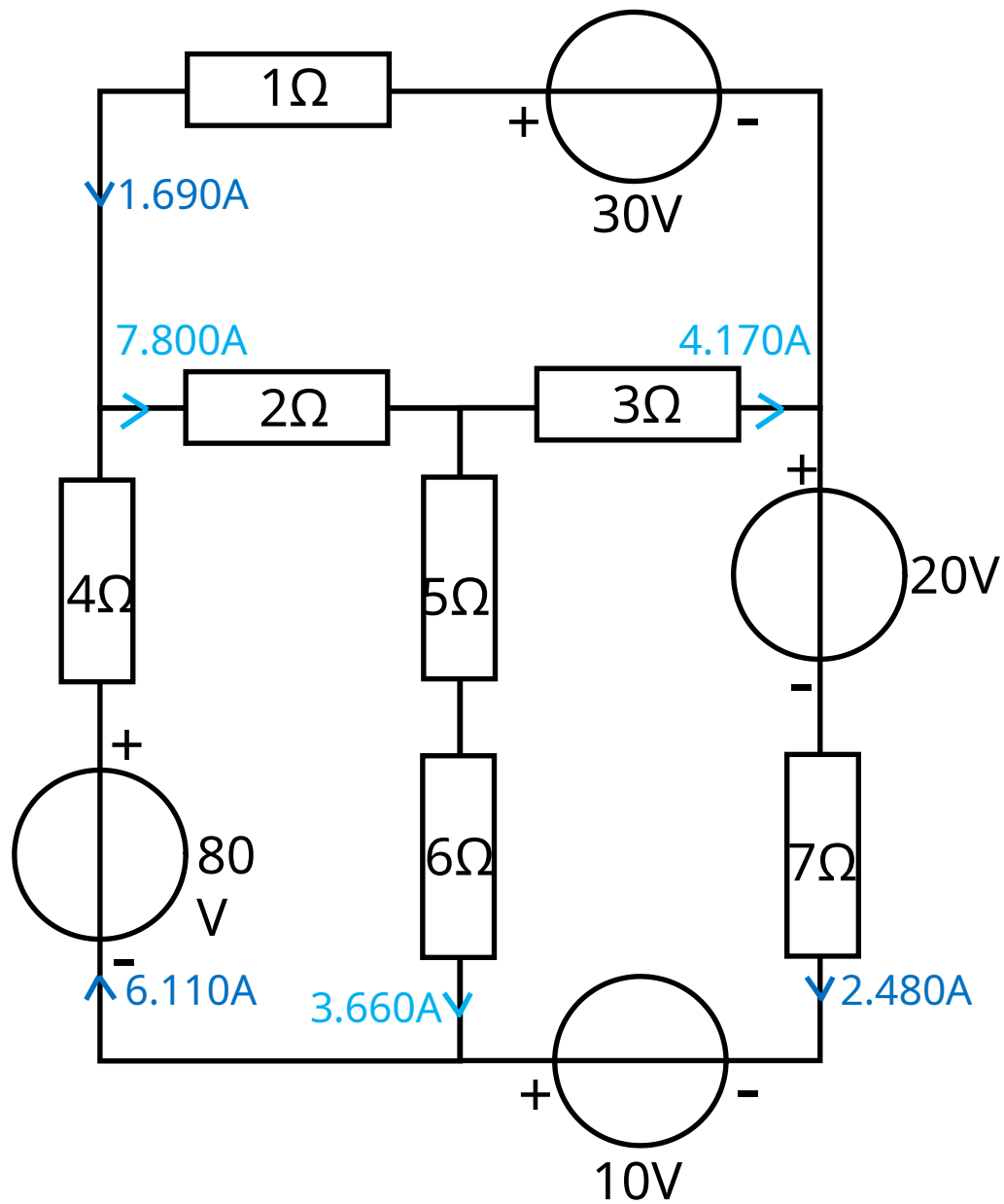
$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0.225 & 0.072 & 0.070 \\ 0.072 & 0.112 & 0.069 \\ 0.070 & 0.069 & 0.094 \end{pmatrix} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} -1.690 \\ 6.110 \\ 2.480 \end{pmatrix} \text{ [A]}$$




$$\begin{aligned}
 -30 &= (1+3+2) I_1 + -2 I_2 + -3 I_3 \\
 80 &= -2 I_1 + (2+5+6+4) I_2 + (-5-6) I_3 \\
 -20 + 10 &= -3 I_1 + (-6-5) I_2 + (3+7+6+5) I_3
 \end{aligned}$$

$$\Rightarrow \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix}^{-1} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix}$$
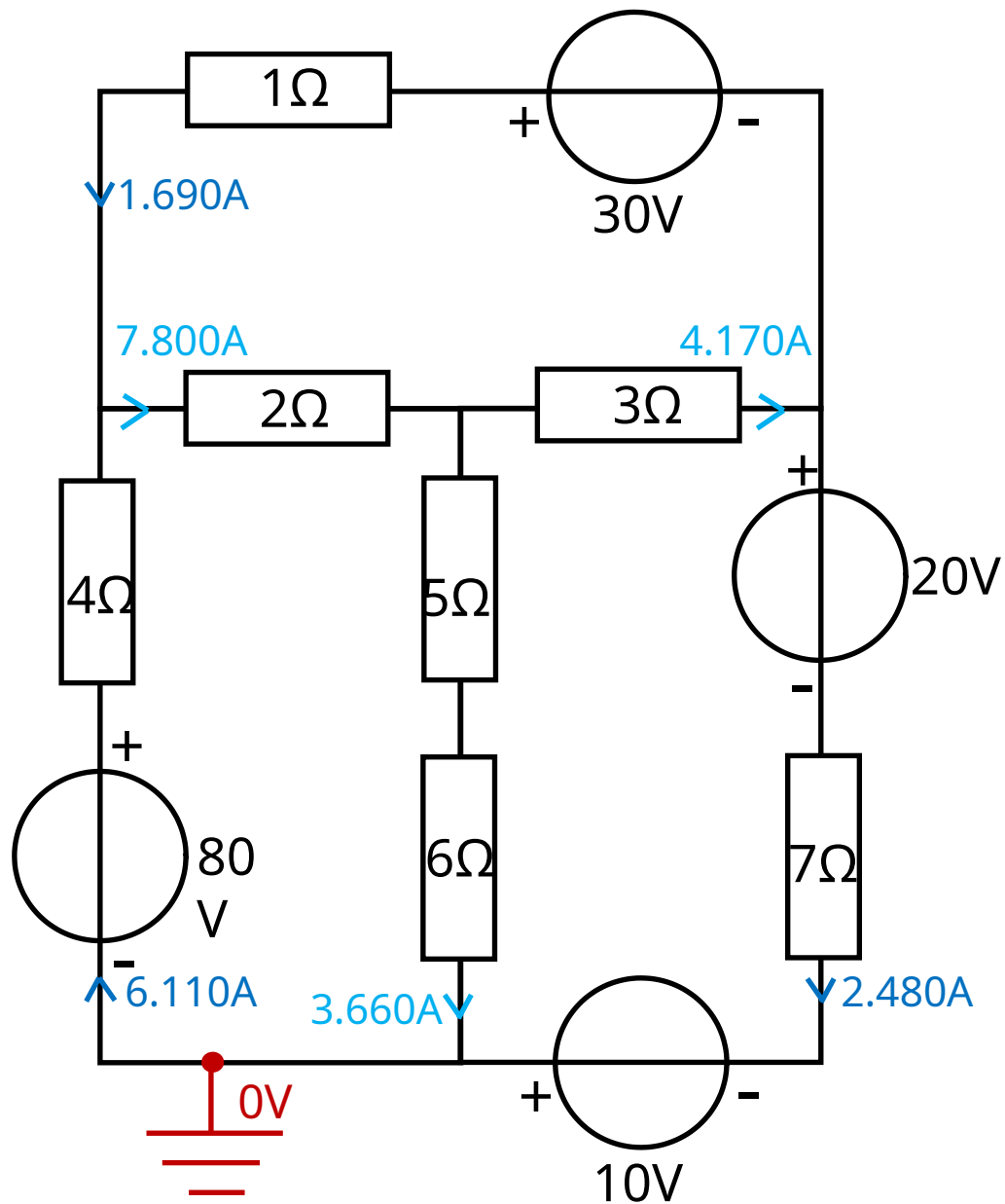
$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0.225 & 0.072 & 0.070 \\ 0.072 & 0.112 & 0.069 \\ 0.070 & 0.069 & 0.094 \end{pmatrix} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} -1.690 \\ 6.110 \\ 2.480 \end{pmatrix} \text{ [A]}$$




$$\begin{aligned}
 -30 &= (1+3+2) I_1 + -2 I_2 + -3 I_3 \\
 80 &= -2 I_1 + (2+5+6+4) I_2 + (-5-6) I_3 \\
 -20 + 10 &= -3 I_1 + (-6-5) I_2 + (3+7+6+5) I_3
 \end{aligned}$$

$$\Rightarrow \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix}^{-1} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix}$$
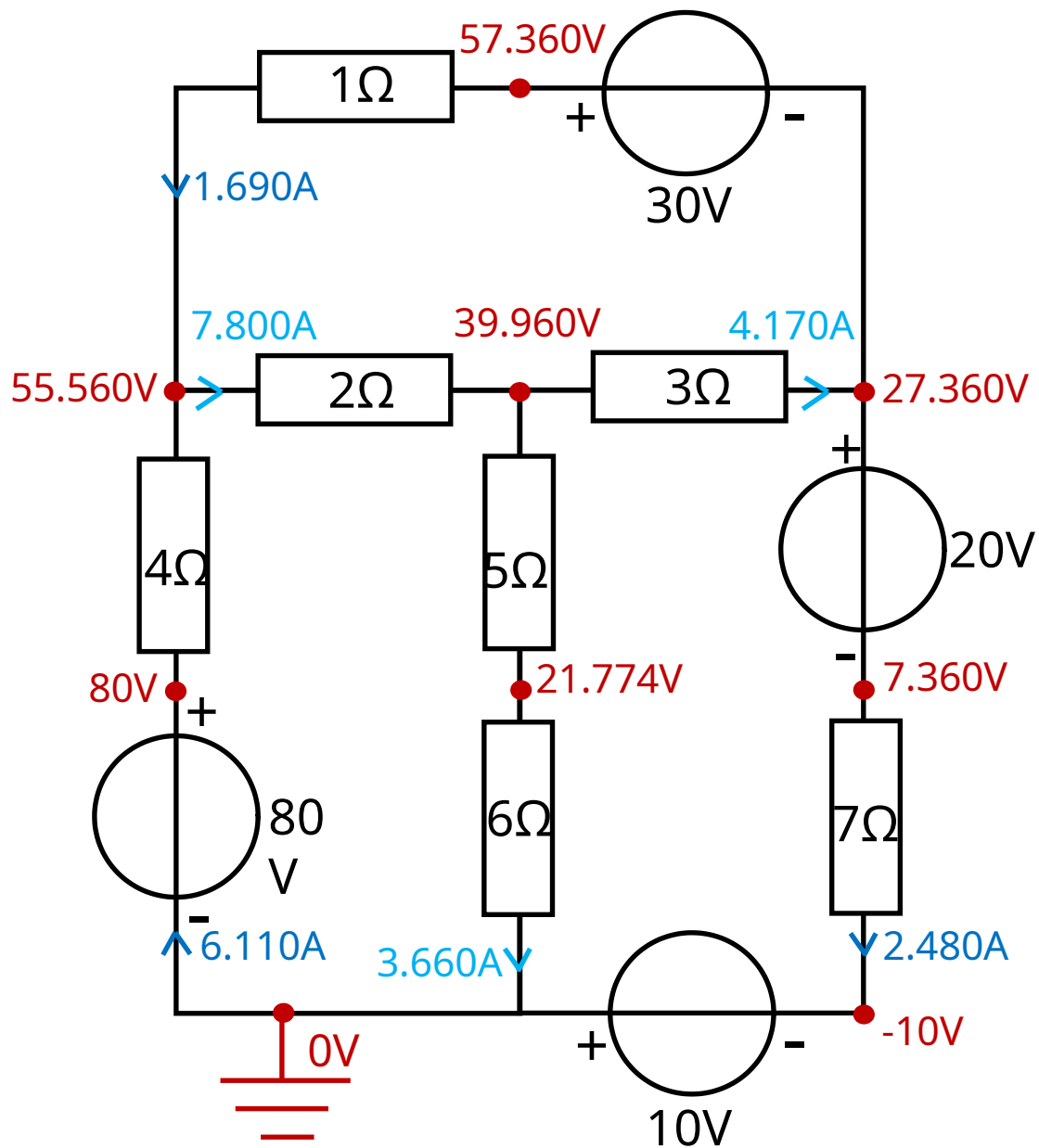
$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0.225 & 0.072 & 0.070 \\ 0.072 & 0.112 & 0.069 \\ 0.070 & 0.069 & 0.094 \end{pmatrix} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} -1.690 \\ 6.110 \\ 2.480 \end{pmatrix} \text{ [A]}$$



$$\begin{aligned}
 -30 &= (1+3+2) I_1 + -2 I_2 + -3 I_3 \\
 80 &= -2 I_1 + (2+5+6+4) I_2 + (-5-6) I_3 \\
 -20 + 10 &= -3 I_1 + (-6-5) I_2 + (3+7+6+5) I_3
 \end{aligned}$$

$$\Rightarrow \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 6 & -2 & -3 \\ -2 & 17 & -11 \\ -3 & -11 & 21 \end{pmatrix}^{-1} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix}$$

$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0.225 & 0.072 & 0.070 \\ 0.072 & 0.112 & 0.069 \\ 0.070 & 0.069 & 0.094 \end{pmatrix} \begin{pmatrix} -30 \\ 80 \\ -10 \end{pmatrix} = \begin{pmatrix} -1.690 \\ 6.110 \\ 2.480 \end{pmatrix} \text{ [A]}$$